

APPENDIX A



EXAMPLE *MATHEMATICA* NOTEBOOKS

Filter Design For Signal Processing

Using **MATLAB** and *Mathematica*

Miroslav D. Lutovac, Ph. D.

Dejan V. Tošić, Ph. D.

Brian L. Evans, Ph. D.

A.1 Analysis by Transform Method of Analog LTI Circuits

Miroslav D. Lutovac, Dejan V. Tasic and Brian L. Evans

lutovac@intel.bg.ac.yu tasic@galeb.etf.bg.ac.yu bevans@ece.utexas.edu

■ A.1.1 References


1. G. S. Moschytz and P. Horn,
Active Filter Design Handbook
For Use with Programmable Pocket Calculators and Mini Computers.
John Wiley and Sons, Ltd., New York, 1981, pp. 38–39
2. R. P. Sallen and E. L. Key,
"A practical method of designing RC active filters,"
IRE Trans. Circuit Theory, CT-2, Mar. 1955, pp. 74–85.
3. D.V. Tasic, M.D. Lutovac, B.L. Evans, I.M. Markoski,
"A tool for symbolic analysis and design of analog active filters,"
5th Int. Workshop, Symbolic Methods, Applications, Circuit Design,
SMACD'98, Kaiserslautern, Germany, pp. 71–74, Oct. 1998.
4. D. V. Tasic, M. D. Lutovac,
"Symbolic computation of impulse, step and sine responses of linear time-invariant systems,"
Proc. 10th Int. Symp. Theor. Electrical Engineering,
ISTET99, Magdeburg, Germany, Sep. 1999, pp. 653–657.
5. D. V. Tasic,
"SALECAS - a package for symbolic analysis of linear circuits and systems,"
4th Int. Workshop, Symbolic Methods, Applications, Circuit Design,
SMACD, Leuven, Belgium, pp. 227–230, Oct. 1996.
6. M. D. Lutovac, D. V. Tasic and B. L. Evans,
"Advanced Filter Design for Signal Processing using MATLAB and Mathematica,"
<http://iritel.iritel.bg.ac.yu/~lutovac/www/afdhome.htm>
<http://galeb.etf.bg.ac.yu/~tasic/afdhome.htm>
<http://www.ece.utexas.edu/~bevans/>

■ A.1.2 Initialization

```
SetDirectory[HomeDirectory[]];
<<Calculus`LaplaceTransform`
<<afd\math\m\clearall.m
<<afd\math\m\drawafil.m
<<afd\math\m\drawacc.m
```

■ A.1.3 Schematic

`DrawLPSK[0, 0, 1/2, 1.25, 8];`

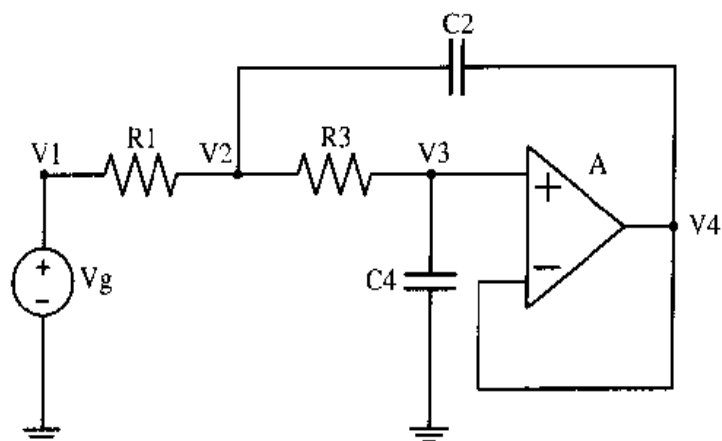

■ A.1.4 Circuit Analysis

■ Reduced Modified Nodal Analysis (RMNA)

```
CircuitEquations = {
  V1 == Vg
  , (V2-V1)/R1 + (V2-V3)/R3 + (V2-V4)*(s*C2) == 0
  , (V3-V2)/R3 + V3*(s*C4) == 0
  , V3 == V4
};
NodeVoltages = {V1,V2,V3,V4};
CircuitResponse = Together[Flatten[
  Solve[CircuitEquations,NodeVoltages]
]];

```

■ A.1.5 Response

```
V1s = Simplify[V1 /. CircuitResponse];
Collect[Numerator[%],s]/Collect[Denominator[%],s]

Vg

V2s = Simplify[V2 /. CircuitResponse];
Collect[Numerator[%],Vg]/Collect[Denominator[%],s]

(1 + C4 R3 s) Vg
-----
1 + (C4 R1 + C4 R3) s + C2 C4 R1 R3 s^2

```

636 App. A Example *Mathematica* Notebooks

```
V3s = Simplify[V3 /. CircuitResponse];
Collect[Numerator[%],s]/Collect[Denominator[%],s]
```

$$\frac{V_g}{1 + (C_4 R_1 + C_4 R_3) s + C_2 C_4 R_1 R_3 s^2}$$

```
V4s = Simplify[V4 /. CircuitResponse];
Collect[Numerator[%],s]/Collect[Denominator[%],s]
```

$$\frac{V_g}{1 + (C_4 R_1 + C_4 R_3) s + C_2 C_4 R_1 R_3 s^2}$$

■ A.1.6 Voltage Transfer Function


```
H = V4s/Vg;
Collect[Numerator[%],s]/Collect[Denominator[%],s]
```

$$\frac{1}{1 + (C_4 R_1 + C_4 R_3) s + C_2 C_4 R_1 R_3 s^2}$$

```
M = Abs[H] /. {C2->4*C, C4->C, R1->R, R3->R} ./ s -> I*2*Pi*f
```

$$\text{Abs}\left[\frac{1}{1 + 4 * C f \text{Pi} R - 16 C F \text{Pi} R^2}\right]$$
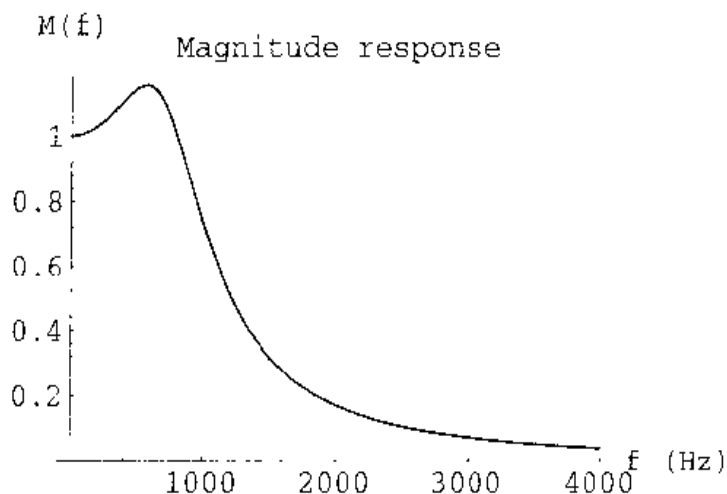
```
Plot[ {M ./ {C->10^(-8), R->10^4}}, {f,0,4000}
, PlotRange -> All
, AxesLabel -> {"f (Hz)", "M(f)"}
, AxesOrigin -> {0,0}
, PlotLabel -> "Magnitude response"];
```




■ A.1.7 Step Response

```
v4t = InverseLaplaceTransform[
H/s /. {C2->4*C, C4->C, R1->R, R3->R}
, s, t];
v4t //Together //Simplify
```

$$1 - \frac{\cos\left[\frac{\sqrt{3} t}{4 C R}\right] - \sin\left[\frac{\sqrt{3} t}{4 C R}\right]}{E \sqrt{3} E}$$
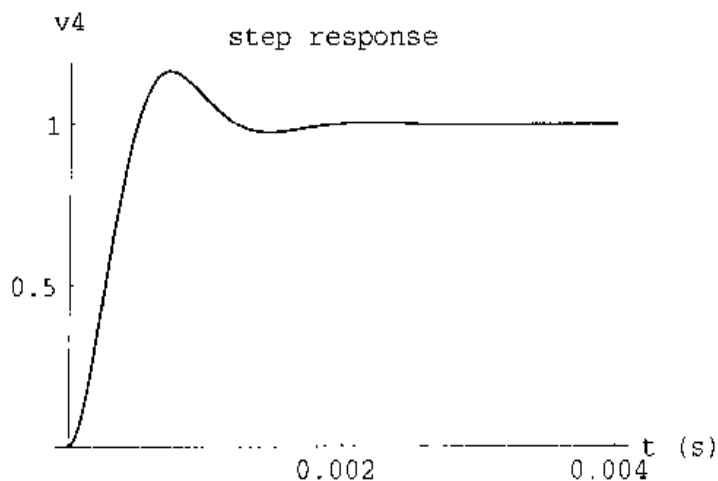
```
Plot[v4t /. {C->10^(-8), R->10^4}
, {t,0,4*10^(-3)}
, PlotRange -> All
, AxesLabel -> {"t (s)", "v4"}
, Ticks -> {{0,0.002,0.004},{0,0.5,1}}
, PlotLabel -> "step response"];
```



A.2 Analysis by Transform Method of Discrete-Time LTI Systems

Miroslav D. Lutovac, Dejan V. Tasic and Brian L. Evans

lutovac@iritel.bg.ac.yu tasic@galeb.etf.bg.ac.yu bevans@ece.utexas.edu

■ A.2.1 References


1. Alan Oppenheim, Ronald Schaffer, "Digital Signal Processing," Prentice-Hall, Englewood Cliffs, New Jersey, 1975.
2. Sanjit Mitra, James Kaiser, "Handbook for Digital Signal Processing," John Wiley, New York, 1993, pp. 127–128.
3. D. V. Tasic, M. D. Lutovac,
"Symbolic computation of impulse, step and sine responses of linear time-invariant systems,"
Proc. 10th Int. Symp. Theor. Electrical Engineering,
ISTET99, Magdeburg, Germany, Sep. 1999, pp. 653–657.
4. John M. Novak and Brian L. Evans,
"Mathematica, Signals and Systems,"
Georgia Tech Research Corp., Atlanta, Georgia, 1995.
5. D. V. Tasic, M. D. Lutovac, and I. M. Markoski,
"Symbolic derivation of transfer functions of discrete-time systems,"
ISTET'97, Palermo, Italia, 9–11 June 1997, pp. 311–314.
6. D. V. Tasic,
"SALECAS - a package for symbolic analysis of linear circuits and systems,"
SMACD, Leuven, Belgium, pp. 227–230, Oct. 1996.
7. M. D. Lutovac, D. V. Tasic and B. L. Evans,
"Advanced Filter Design for Signal Processing using MATLAB and Mathematica,"
<http://iritel.iritel.bg.ac.yu/~lutovac/www/afdhhome.htm>
<http://galeb.etf.bg.ac.yu/~tasic/afdhhome.htm>
<http://www.ece.utexas.edu/~bevans/>

■ A.2.2 Initialization

```
SetDirectory[HomeDirectory[]];
<<afd\math\m\clearall.m
AppendTo[$Path, "APPS"];
Needs["SignalProcessing`Master`"]
<<afd\math\m\drawdfil.m
<<afd\math\m\drawiirf.m
```

■ A.2.3 Block Diagram

`DrawTDF2[0,0,1,1/0.8,10];`

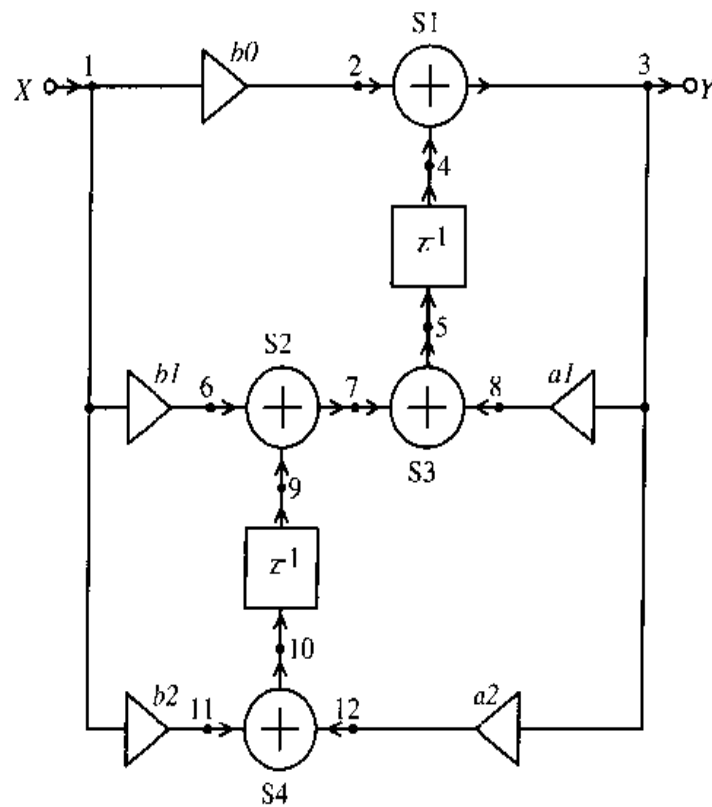

■ A.2.4 Analysis (v=1/z)

```
ElementEquations = {
  Y1 == X
, Y2 == b0*Y1 + Xb0
, Y3 == Y2 + Y4
, Y4 == v*Y5
, Y5 == Y7 + Y8
, Y6 == b1*Y1 + Xb1
, Y7 == Y6 + Y9
, Y8 == a1*Y3 + Xa1
, Y9 == v*Y10
, Y10 == Y11 + Y12
, Y11 == b2*Y1 + Xb2
, Y12 == a2*Y3 + Xa2
};
```

```
NodeSignals = {Y1,Y2,Y3,Y4,Y5,Y6,Y7,Y8,Y9,Y10,Y11,Y12};
Response = Flatten[Solve[ElementEquations,NodeSignals]];
Y = Together[Y3/.Response]
```

$$\frac{-(b_0 X^2 - b_1 v X - b_2 v^2 X^2 - v X a_1 - v^2 X a_2 - X b_0 - v X b_1 - v^2 X b_2)}{-1 + a_1 v + a_2 v^2}$$

■ A.2.5 Transfer Function and Noise Transfer Functions

```
Hv = Y /. {X -> 1, Xa1 -> 0, Xa2 -> 0, Xb0 -> 0, Xb1 -> 0, Xb2 -> 0};
Halv = Y /. {X -> 0, Xa1 -> 1, Xa2 -> 0, Xb0 -> 0, Xb1 -> 0, Xb2 -> 0};
Ha2v = Y /. {X -> 0, Xa1 -> 0, Xa2 -> 1, Xb0 -> 0, Xb1 -> 0, Xb2 -> 0};
Hb0v = Y /. {X -> 0, Xa1 -> 0, Xa2 -> 0, Xb0 -> 1, Xb1 -> 0, Xb2 -> 0};
Hb1v = Y /. {X -> 0, Xa1 -> 0, Xa2 -> 0, Xb0 -> 0, Xb1 -> 1, Xb2 -> 0};
Hb2v = Y /. {X -> 0, Xa1 -> 0, Xa2 -> 0, Xb0 -> 0, Xb1 -> 0, Xb2 -> 1};
H = Collect[-Numerator[Hv],v] / (-Collect[Denominator[Hv],v]);
Hal = Collect[-Numerator[Halv],v]/(-Collect[Denominator[Halv],v]);
Ha2 = Collect[-Numerator[Ha2v],v]/(-Collect[Denominator[Ha2v],v]);
Hb0 = Collect[-Numerator[Hb0v],v]/(-Collect[Denominator[Hb0v],v]);
Hb1 = Collect[-Numerator[Hb1v],v]/(-Collect[Denominator[Hb1v],v]);
Hb2 = Collect[-Numerator[Hb2v],v]/(-Collect[Denominator[Hb2v],v]);
v2invz = {v->z^"-1", v^2->z^("2")};
Print["H(z) = ", H /. v2invz ]
Print["Hal(z) = ", Hal /. v2invz ]
Print["Ha2(z) = ", Ha2 /. v2invz ]
Print["Hb0(z) = ", Hb0 /. v2invz ]
Print["Hb1(z) = ", Hb1 /. v2invz ]
Print["Hb2(z) = ", Hb2 /. v2invz ]
```

$$H(z) = \frac{b_0 + b_1 z^{-1} + b_2 z^{-2}}{1 - a_1 z^{-1} - a_2 z^{-2}}$$

$$Hal(z) = \frac{z}{1 - a_1 z^{-1} - a_2 z^{-2}}$$

$$Ha2(z) = \frac{z^2}{1 - a_1 z^{-1} - a_2 z^{-2}}$$

$$Hb0(z) = \frac{1}{1 - a1 z^{-1} - a2 z^{-2}}$$

$$Hb1(z) = \frac{z}{1 - a1 z^{-1} - a2 z^{-2}}$$

$$Hb2(z) = \frac{z^2}{1 - a1 z^{-1} - a2 z^{-2}}$$

■ A.2.6 Complex Response in Terms of $v=z^{-1}$

`Y3z = Collect[-Numerator[Y],X]/(-Denominator[Y])`

$$\frac{(b0 + b1 v + b2 v^2) X^2 + v X a1 + v^2 X a2 + X b0 + v X b1 + v^2 X b2}{1 - a1 v - a2 v^2}$$

■ A.2.7 Transfer Function

`H3z = H /. {b0->1, b1->2, b2->1, a1->0, a2->-1/2, v->z^{-1}}`

$$\frac{1 + z^{-2}}{1 + \frac{1}{2} z^{-2}}$$

■ A.2.8 Impulse Response

`y3n = InverseZTransform[H3z,z,n]`

$$\frac{-\left(\frac{1}{\sqrt{2}}\right)^n (1 - 2 I \sqrt{2}) \text{DiscreteStep}[n]}{2} + \frac{\left(\frac{1}{\sqrt{2}}\right)^n (1 + 2 I \sqrt{2}) \text{DiscreteStep}[n]}{2} + 2 \text{KroneckerDelta}[n]$$

642 App. A Example *Mathematica* Notebooks

```
y3nDS = ComplexExpand[Coefficient[y3n,DiscreteStep[n]]]
```

$$\begin{aligned} & \cos\left[\frac{n\pi}{2}\right] \\ & -\left(\frac{1/2 - n/2}{2}\right) + 2 \sin\left[\frac{n\pi}{2}\right] \end{aligned}$$


```
y3nKD = Coefficient[y3n,KroneckerDelta[n]]
```

```
2
```

```
h3n = y3nDS*DiscreteStep[n] + y3nKD*KroneckerDelta[n]
```

$$\begin{aligned} & \cos\left[\frac{n\pi}{2}\right] \\ & 2 \text{KroneckerDelta}[n] + \text{DiscreteStep}[n] \left(-\left(\frac{1/2 - n/2}{2}\right) + 2 \sin\left[\frac{n\pi}{2}\right] \right) \end{aligned}$$
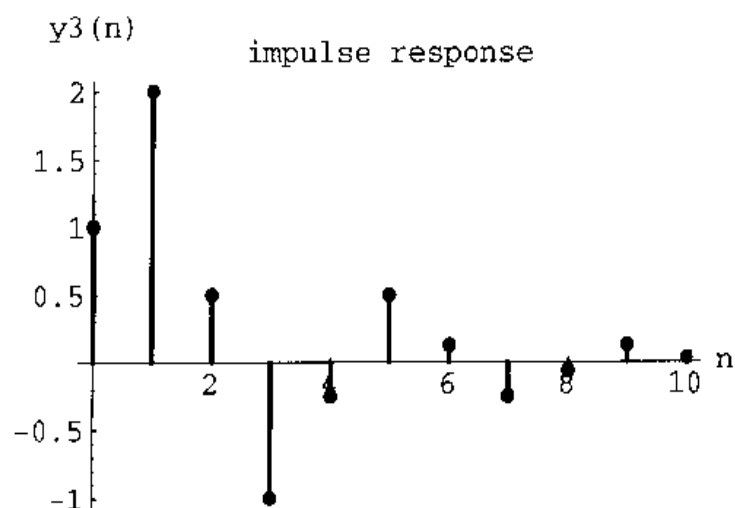
```
DiscreteSignalPlot[h3n
,{n,0,10}
,AxesLabel -> {"n","y3(n)"}
,PlotLabel -> "impulse response"
];
```



```
Table[{n,h3n}, {n,0,10}]
```

```
% //TableForm //N
```

```

      1      1      1      1      1
{0, 1}, {1, 2}, {2, -}, {3, -1}, {4, -(-)}, {5, -}, {6, -}, {7, -(-)},
      2      4      2      8      4

```

```

      1      1      1
{8, -(-)}, {9, -}, {10, --}}
      16      8      32

```

```

0      1.
1.     2.
2.     0.5
3.     -1.
4.     -0.25
5.     0.5
6.     0.125
7.     -0.25
8.     -0.0625
9.     0.125
10.    0.03125

```

A.3 Switched Capacitor Filter - Mode 3a

Analysis and Design

Miroslav D. Lutovac, Dejan V. Tasic and Brian L. Evans

lutovac@iritel.bg.ac.yu tasic@galeb.etf.bg.ac.yu bevans@ece.utexas.edu

■ A.3.1 References


1. Linear Technology Corporation
Monolithic Filter Handbook, 1990.
2. M. D. Lutovac, D. Novakovic, I. Markoski,
"Selective SC-filters with low passive sensitivity,"
Electronics Letters vol. 33, no. 8, pp. 674–675, Apr. 1997.
3. M.D.Lutovac, D. V. Tasic, D.Novakovic,
"Programmable low-pass/high-pass SC-filters,"
Proc.9th Conf. MELECON '98, Tel-Aviv, Israel May 1998, pp.673–677
4. D.V. Tasic, M.D. Lutovac, B.L. Evans, I.M. Markoski,
"A tool for symbolic analysis and design of analog active filters,"
5th Int. Workshop, Symbolic Methods, Applications, Circuit Design,
SMACD'98, Kaiserslautern, Germany, pp. 71–74, Oct. 1998.
5. M. D. Lutovac, D. V. Tasic and B. L. Evans,
"Advanced Filter Design for Signal Processing using MATLAB and Mathematica,"
<http://iritel.iritel.bg.ac.yu/~lutovac/www/afdhome.htm>
<http://galeb.etf.bg.ac.yu/~tasic/afdhome.htm>
<http://www.ece.utexas.edu/~bevans/>

■ A.3.2 Initialization

```
SetDirectory[HomeDirectory[]];
<<afd\math\m\clearall.m
<<afd\math\m\drawafil.m
<<afd\math\m\drawasc.m
```

■ A.3.3 Schematic

```
DrawMode3a[0,0,1/2,1/0.8,8];
```

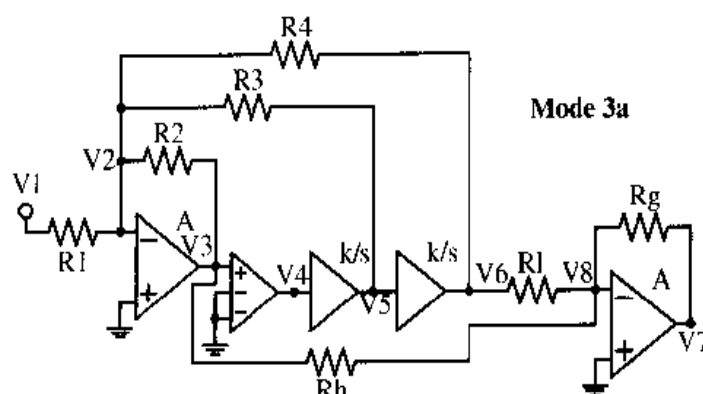

■ A.3.4 Circuit Analysis

■ Reduced Modified Nodal Analysis

```
CircuitEquations = {
  V1 == Vg
, (V2-V1)/R1 + (V2-V3)/R2 + (V2-V5)/R3 + (V2-V6)/R4 == 0
, V3 == -A*V2
, V4 == V3
, V5 == V4*k/s
, V6 == V5*k/s
, (V8-V6)/R1 + (V8-V3)/Rh + (V8-V7)/Rg == 0
, V7 == -A*V8
};
NodeVoltages = {V1,V2,V3,V4,V5,V6,V7,V8};
CircuitResponse = Together[Flatten[
  Solve[CircuitEquations,NodeVoltages]
]];
Print["V1 = ", V1 /. CircuitResponse]
Print["V7 = ", V7 /. CircuitResponse]
```

$$V1 = Vg$$

$$V7 = -\frac{(A^2 R_2 R_3 R_4 s^2 (-(k R_g R_h) - R_g R_l s) Vg)}{((R_g R_h + R_g R_l + R_h R_l + A R_h R_l) ((R_1 R_2 R_3 + R_1 R_2 R_4 + R_1 R_3 R_4 + R_2 R_3 R_4) s^3 - A (-(k R_1 R_2 R_3 s) + s (-(k R_1 R_2 R_4) - R_1 R_3 R_4 s))))}$$

■ A.3.5 Voltage Transfer Function

```
H = V7/V1 /. CircuitResponse //Together //Simplify;
H3a = Limit[H, A->Infinity];
Print["H(s) = ",
  Factor[Collect[Numerator[H3a],s]]/Factor[Collect[Denominator[H3a],s]]
]
```

$$H(s) = \frac{R_g R_2 R_3 R_4 (k^2 R_h + R_l^2 s^2)}{R_h R_l R_1 (k^2 R_2 R_3 + k^2 R_2 R_4 s + R_3 R_4 s^2)}$$

■ A.3.6 Definitions and Procedures

```
PoleQpole[H,s_] := Module[{den,fp,Qp},
  den = Denominator[H];
  fp = Sqrt[Coefficient[den,s,0]/Coefficient[den,s,2]]/(2*Pi);
  Qp = (Coefficient[den,s,2]/Coefficient[den,s,1])*(2*Pi*fp);
  Simplify[{fp, Qp}];
```

```
ZeroQzero[H_,s_] := Module[{fz,num,Qz0},
  num = Numerator[H];
  Qz0 = (Coefficient[num,s,2]/Coefficient[num,s,1]);
  fz = Sqrt[Coefficient[num,s,0]/Coefficient[num,s,2]]/(2*Pi);
  Simplify[{fz, Qz0*fz}];
Sensitivity[F_,x_] := (x/F)*D[F,x];
GSP[F_,A_] := Limit[A*Sensitivity[F,A],A->Infinity]//Simplify;
PrintLabeledList[expressions_List,labels_List] := Map[
  Print[#[[1]]," = ",#[[2]]]&
,Transpose[{labels,expressions}]
];
```

■ A.3.7 Poles, Zeros, Q-Factors

```
{fp,Qp} = Simplify[PoleQpole[H,s]];
PrintLabeledList[{fp,Qp},{ "fp","Qp"}];
```

$$fp = \frac{\sqrt{\frac{A^2 k^2 R_1^2 R_2^2 R_3^2}{R_1^2 R_2^2 R_3^2 + R_1^2 R_2^2 R_4^2 + R_1^2 R_3^2 R_4^2 + A^2 R_1^2 R_3^2 R_4^2 + R_2^2 R_3^2 R_4^2}}}{2 \pi \sqrt{\frac{A^2 k^2 R_1^2 R_2^2 R_3^2}{R_1^2 R_2^2 R_3^2 + R_1^2 R_2^2 R_4^2 + R_1^2 R_3^2 R_4^2 + A^2 R_1^2 R_3^2 R_4^2 + R_2^2 R_3^2 R_4^2}}}$$

```
fp0 = Limit[fp, A -> Infinity];
Qp0 = Simplify[Limit[Qp, A -> Infinity]/.k->1];
PrintLabeledList[{fp0,Qp0},{ "fp","Qp"}];
```

$$fp = \frac{\sqrt{\frac{k^2 R_2^2}{R_4^2}}}{2 \pi \sqrt{\frac{R_2^2 R_3^2 \sqrt{\frac{k^2 R_2^2}{R_4^2}}}{R_4^2}}}$$

$$Qp = \frac{R_2}{R_2}$$

```
{fz,Qz} = Simplify[ZeroQzero[H,s]];
PrintLabeledList[{fz,Qz},{"fz","Qz"}];

1
Power::infy: Infinite expression - encountered.
0

2
k Rh
Sqrt[-----]
R1
fz = -----
2 Pi
Qz = ComplexInfinity
```

■ A.3.8 Gain-Sensitivity Product (GSP)

```
GSPfp = GSP[fp,A];
GSPQp = GSP[Qp,A];
PrintLabeledList[{GSPfp,GSPQp},{"GSPfp","GSPQp"}];
```

```
GSPfp = - + ---- + ---- + ----
2 2 R1 2 R3 2 R4
1 R2 R2 R2
GSPQp = -(-) - ---- - ---- - ----
2 2 R1 2 R3 2 R4
```

■ A.3.9 Design

■ Find Element Values

```
DesignMode3a[K_,Qp_,wp_,wz_,fc1k_,P_:100,R1_:R1nom,R2_:R2nom,Rh_:Rhnom]:=
Module[{R3,R4,R1,Rg},
R4 = R2*(2*Pi*fc1k/(P*wp))^2;
R3 = Qp*Sqrt[R2*R4];
R1 = Rh*(2*Pi*fc1k/(P*wz))^2;
Rg = K*Rh*R1/R2;
{R1,R2,R3,R4,R1,Rh,Rg}
];
{R1,R2,R3,R4,R1,Rh,Rg} = Together[
DesignMode3a[K,Q,W,Z,Fc,P,R1n,R2n,Rhn]];
PrintLabeledList[{R1,R2,R3,R4,R1,Rh,Rg}
,{"R1","R2","R3","R4","R1","Rh","Rg"}];
```

```
R1 = R1n
R2 = R2n

2 2 2
Fc Pi R2n
R3 = 2 Q Sqrt[-----]
2 2
P W
```

648 App. A Example *Mathematica* Notebooks

$$R4 = \frac{\frac{2}{4} \frac{2}{Fc} \frac{2}{Pi} \frac{2}{R2n}}{\frac{2}{P} \frac{2}{W} \frac{2}{2} \frac{2}{4} \frac{2}{Fc} \frac{2}{Pi} \frac{2}{Rhn}}$$

$$R1 = \frac{\frac{2}{2} \frac{2}{P} \frac{2}{Z}}{Rh = Rhn}$$

$$K Rhn R1n$$

$$Rg = \frac{R2n}{R2n}$$

■ Test

```
H3atest = Simplify[ExpandAll[Together[Limit[H , A -> Infinity]] /.
{Sqrt[x.^2*y.^2/z.^2] -> x*y/z, Sqrt[x.^2*y.^2*p.^2/z.^2] -> x*y*p/z
, Sqrt[x.^2*y.^2*p.^2/(z.^2*n.^2)] -> x*y*p/(z*n)} ]];
num = Numerator[H3atest];
den = Denominator[H3atest];
numlist = CoefficientList[num,s];
denlist = CoefficientList[den,s];
K3at =(numlist[[3]]/denlist[[3]]);
H3at = K3at *
Simplify[num/numlist[[3]]]/Simplify[den/denlist[[3]]] /. k-> 2*Pi*Fc/P
```

$$K (s^2 + Z^2)$$

$$\frac{2}{s} + \frac{s^2 W}{Q} + W^2$$

■ Design Examples

```

values = {K -> 1, Q -> 1.0349, W -> 2*Pi*1710.9457, Z -> 2*Pi*5129.3034
, Fc -> 256.*10^3, P -> 100, R12 -> 23.16*10^3
, R22 -> 10.*10^3, Rh2 -> 238.6*10^3} //N;
h1 = H /. k -> 2*Pi*Fc/P /. values //N;
H3atest = Limit[h1, A -> Infinity];
H3atest = H3atest /. Sqrt[x^2] -> x;
num = Numerator[H3atest];
den = Denominator[H3atest];
numlist = CoefficientList[num, s];
denlist = CoefficientList[den, s];
K3at = (numlist[[3]]/denlist[[3]]);
H3at = K3at * Simplify[num/numlist[[3]]]/Simplify[den/denlist[[3]]]

```

$$\frac{1. (1.03867 \cdot 10^9 + 1. s^2)}{1.15567 \cdot 10^8 + 10387.7 s + 1. s^2}$$

```

Rexample1 = N[{R1, R2, R3, R4, R1, Rh, Rg} /. values] /. Sqrt[R2n^2] -> R2n;
PrintLabeledList[Rexample1, {"R1", "R2", "R3", "R4", "R1", "Rh", "Rg"}];

```

```


R1 = R1n
R2 = R2n
R3 = 1.54847 R2n
R4 = 2.23876 R2n
R1 = 0.249094 Rhn
Rh = Rhn
1. Rhn R1n
Rg = -----
      R2n

```

```

Plot[{Abs[H3at] /. s -> I*2*Pi*f}
, {f, 100, 10000}
, PlotRange -> All
, Ticks -> {{0, 2000, 5000, 10000}, {0, 2, 4, 6, 8, 10}}
, AxesLabel -> {"f (Hz)", "M(f)"}
];

```

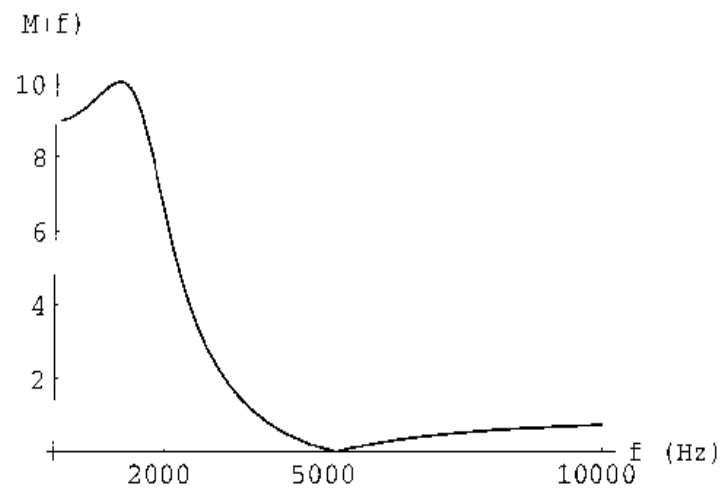

■ A.3.10 Optimization

■ Find R_2/R_1 for Low Gain-Sensitivity Product

```
sf = (Simplify[N[Together[GSPfp /. values]]
      /. Sqrt[x_^2] -> x/. Sqrt[x_^2*y_^2] -> x*y ]
      /. Sqrt[R2n^2] -> R2n)
```

```
0.5 R2n
1.04624 + -----
          R1n
```

■ Remark

We have to choose $R_1 > R_2$ to minimize GSP.

A.4 OTA-C General Biquad

Analysis and Design

Miroslav D. Lutovac, Dejan V. Tasic and Brian L. Evans

lutovac@iritel.bg.ac.yu tasic@galeb.etf.bg.ac.yu bevans@ece.utexas.edu

■ A.4.1 References


1. Wai-Kai-Chen, Ed.,
"The Circuits and Filters Handbook," p. 2479,
"CRC Press," "Boca Raton, Florida," "1995."
2. D.V. Tasic, M.D. Lutovac, B.L. Evans, I.M. Markoski,
"A tool for symbolic analysis and design of analog active filters,"
5th Int. Workshop, Symbolic Methods, Applications, Circuit Design,
SMACD'98, Kaiserslautern, Germany, pp. 71–74, Oct. 1998.
3. M. D. Lutovac, D. V. Tasic and B. L. Evans,
"Advanced Filter Design for Signal Processing using MATLAB and Mathematica,"
<http://iritel.iritel.bg.ac.yu/lutovac/www/afdhome.htm>
<http://galeb.etf.bg.ac.yu/tasic/afdhome.htm>
<http://www.ece.utexas.edu/bevans/>

■ A.4.2 Initialization

```
SetDirectory[HomeDirectory[]];
<<afd\math\m\cTeaara11.m
<<afd\math\m\drawafil.m
<<afd\math\m\drawaota.m
```

■ A.4.3 Schematic

```
DrawOTAb[0, 0, 1/2, 1/08, 8]
```

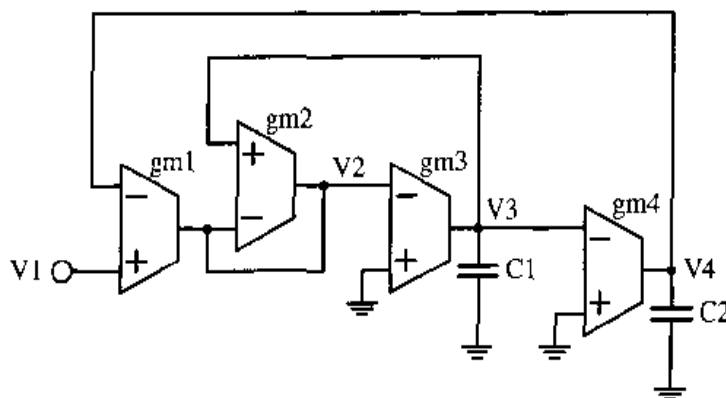

■ A.4.4 Circuit Analysis

■ Reduced Modified Nodal Analysis

```
CircuitEquations = {
  V1 == Vg
, -(V1-V4)*gm1 - (V3-V2)*gm2 == 0
, -(-V2)*gm3 + V3/(1/(s*C1)) == 0
, -(-V3)*gm4 + V4/(1/(s*C2)) == 0
};

NodeVoltages = {V1,V2,V3,V4};
CircuitResponse = Together[Flatten[
  Solve[CircuitEquations,NodeVoltages]
]];

```

■ A.4.5 Voltage Transfer Function

```
H = V4/V1 /. CircuitResponse //Together //Simplify;
Print["H(s) = ", H]
Hhp = V2/V1 /. CircuitResponse //Together //Simplify;
Print["Hhp(s) = ", Hhp]
Hbp = V3/V1 /. CircuitResponse //Together //Simplify;
Print["Hbp(s) = ", Hbp]

```

$$H(s) = \frac{gm1 \ gm3 \ gm4}{gm1 \ gm3 \ gm4 + C2 \ gm2 \ gm3 \ s + C1 \ C2 \ gm2 \ s^2}$$

$$Hhp(s) = \frac{C1 \ C2 \ gm1 \ s}{gm1 \ gm3 \ gm4 + C2 \ gm2 \ gm3 \ s + C1 \ C2 \ gm2 \ s^2}$$

$$Hbp(s) = -\left(\frac{C2 \ gm1 \ gm3 \ s}{gm1 \ gm3 \ gm4 + C2 \ gm2 \ gm3 \ s + C1 \ C2 \ gm2 \ s^2}\right)$$

■ A.4.6 Definitions and Procedures

```
PoleQpole[H_,s_] := Module[{den,fp,Qp},
  den = Denominator[H];
  fp = Sqrt[Coefficient[den,s,0]/Coefficient[den,s,2]]/(2*Pi);
  Qp = (Coefficient[den,s,2]/Coefficient[den,s,1])*(2*Pi*fp);
  Simplify[{fp, Qp}]];
ZeroQzero[H_,s_] := Module[{fz,num,Qz0},
  num = Numerator[H];
  Qz0 = (Coefficient[num,s,2]/Coefficient[num,s,1]);
  fz = Sqrt[Coefficient[num,s,0]/Coefficient[num,s,2]]/(2*Pi);
  Simplify[{fz, Qz0*fz}]];

```

```
PrintLabeledList[expressions_List, labels_List] := Map[
  Print[#[[1]], " = ", #[[2]]]&
, Transpose[{labels, expressions}]
];
```

■ A.4.7 Poles, Zeros, Q-Factors

```
{fp, Qp} = Simplify[PoleQpole[H, s]];
Klp = H /. s -> 0
PrintLabeledList[{fp, Qp}, {"fp", "Qp"}];
```

```
1
      gm1 gm3 gm4
      Sqrt[-----]
      C1 C2 gm2
fp = -----
      2 Pi
      gm1 gm3 gm4
      C1 Sqrt[-----]
      C1 C2 gm2
Qp = -----
      gm3
```

■ A.4.8 Design

■ Find Element Values

```
DesignOTA1[Qp_, wp_, C1_, C2_, gm1_, gm2_] :=
  Module[{gm3, gm4},
    gm3 = C1*wp/Qp;
    gm4 = C2*wp*Qp*gm2/gm1;
    {C1, C2, gm1, gm2, gm3, gm4}
  ];
{C1, C2, gm1, gm2, gm3, gm4} = Together[DesignOTA1[Q, W, c1, c2, g1, g2]];
PrintLabeledList[{C1, C2, gm1, gm2, gm3, gm4}, {"C1", "C2", "gm1", "gm2", "gm3", "gm4"}];
```

```
C1 = c1
C2 = c2
gm1 = g1
gm2 = g2
      c1 W
gm3 = ----
      Q
      c2 g2 Q W
gm4 = -----
      g1
```

A.4.9 Test

Simplify[H]

$$\frac{Q^2 W^2}{Q^2 s^2 + s^2 W^2 + Q^2 W^2}$$

Design Examples

```
values = {Q -> 4., W -> N[2*Pi*10^6] ,
  c1 -> 10.*10^(-12), c2 -> 10.*10^(-12), g1 -> g , g2 -> g} //N;
h1 = Together[H /. values] /. 1. -> 1;
Print["gm3 = ", 10^3*gm3 /. values, " mS "]
Print["gm4 = ", 10^3*gm4 /. values, " mS "]
h = (Numerator[h1]/g)/ (Simplify[Denominator[h1]/g])
```

gm3 = 0.015708 mS

gm4 = 0.251327 mS

$$\frac{3.94784 \cdot 10^{13}}{3.94784 \cdot 10^{13} + 1.5708 \cdot 10^6 s^2 + s^2}$$

```
PrintLabeledList[N[{Q,W/(2*Pi)} /. values]
```

```
, {"Qp", "fp (Hz)"}];
```

```
Print["-----"]
```

```
Rexample1 = N[{C1*10^(12), C2*10^(12), gm1, gm2, gm3*10^(3), gm4*10^(3)} /. values] ;
```

```
PrintLabeledList[Rexample1
```

```
, {"C1 (pF)", "C2 (pF)", "gm1", "gm2", "gm3 (mS)", "gm4 (mS)"}];
```

Qp = 4.

fp (Hz) = 1. 10⁶

C1 (pF) = 10.

C2 (pF) = 10.

gm1 = g

gm2 = g

gm3 (mS) = 0.015708

gm4 (mS) = 0.251327


```
Plot[{Abs[h] /. s -> I*2*Pi*f*10^6}
```

```
, {f, 0.01, 4}
```

```
, PlotRange -> All
```

```
, AxesLabel -> {"f (MHz)", "M(f)"}]
```

```
];
```

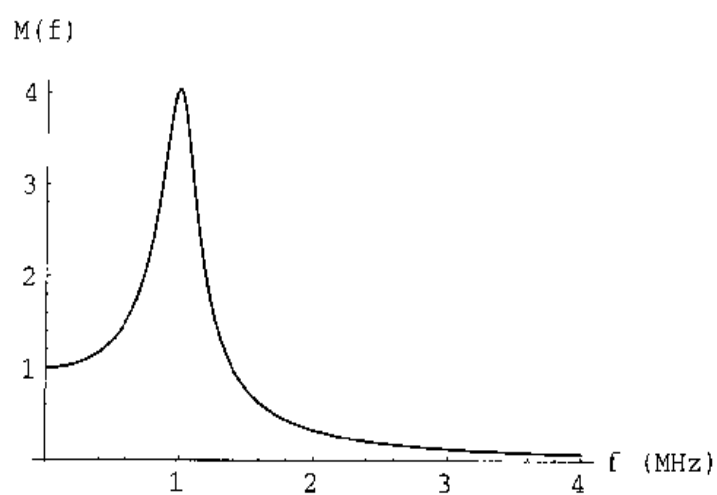

A.5 Lowpass-Medium-Q-Factor Active RC Filter Analysis and Design

Miroslav D. Lutovac, Dejan V. Tasic and Brian L. Evans

lutovac@iritel.bg.ac.yu tasic@galeb.etf.bg.ac.yu bevans@ece.utexas.edu

■ A.5.1 References


1. G. S. Moschytz and P. Horn,
Active Filter Design Handbook
For Use with Programmable Pocket Calculators and Mini Computers
John Wiley and Sons, Ltd., New York, 1981, pp. 38–39.
2. R. P. Sallen and E. L. Key,
“A practical method of designing RC active filters,”
IRE Trans. Circuit Theory, CT-2, Mar. 1955, pp. 74–85.
3. D.V. Tasic, M.D. Lutovac, B.L. Evans, I.M. Markoski,
“A tool for symbolic analysis and design of analog active filters,”
5th Int. Workshop, Symbolic Methods, Applications, Circuit Design,
SMACD’98, Kaiserslautern, Germany, pp. 71–74, Oct. 1998.
4. M. D. Lutovac, D. V. Tasic and B. L. Evans,
“Advanced Filter Design for Signal Processing using MATLAB and Mathematica,”
<http://iritel.iritel.bg.ac.yu/~lutovac/www/afdhome.htm>
<http://galeb.etf.bg.ac.yu/~tasic/afdhome.htm>
<http://www.ece.utexas.edu/~bevans/>

■ A.5.2 Initialization

```
SetDirectory[HomeDirectory[]];
<<afd\math\m\clearall.m
<<afd\math\m\drawafil.m
<<afd\math\m\drawarc.m
```


■ A.5.3 Schematic

`DrawLPMQ[0,0,1/2,1/0.8];`

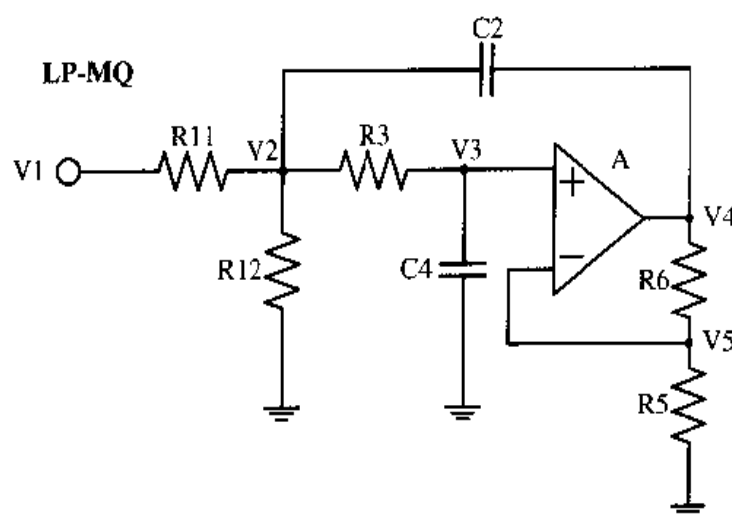

■ A.5.4 Circuit Analysis

■ Reduced Modified Nodal Analysis

```
CircuitEquations = {V1 == Vg
, (V2-V1)/R11 + V2/R12 + (V2-V3)/R3 + (V2-V4)/(1/(s*C2)) == 0
, (V3-V2)/R3 + V3/(1/(s*C4)) == 0
, (V5-V4)/R6 + V5/R5 == 0
, (V3-V5)*A == V4};
NodeVoltages = {V1,V2,V3,V4,V5};
CircuitResponse = Together[Flatten[
  Solve[CircuitEquations,NodeVoltages]
]];
Print["V1 = ", V1 /. CircuitResponse]
Print["V4 = ", V4 /. CircuitResponse]
```

$V1 = Vg$

$V4 = -((A \ R12 \ R3 \ R5 \ Vg) /$

$\begin{aligned} & (A \ C2 \ R11 \ R12 \ R3 \ R5 \ s - (-R5 - A \ R5 - R6) (1 + C4 \ R3 \ s) \\ & (R11 \ R12 + R11 \ R3 + R12 \ R3 + C2 \ R11 \ R12 \ R3 \ s) + \\ & (-R5 - A \ R5 - R6) (R11 \ R12 + A \ C2 \ R11 \ R12 \ R3 \ s))) - \\ & (A \ R12 \ R3 \ (-R5 - A \ R5 - R6) \ Vg) / \end{aligned}$

$\begin{aligned} & (A \ C2 \ R11 \ R12 \ R3 \ R5 \ s - (-R5 - A \ R5 - R6) (1 + C4 \ R3 \ s) \\ & (R11 \ R12 + R11 \ R3 + R12 \ R3 + C2 \ R11 \ R12 \ R3 \ s) + \\ & (-R5 - A \ R5 - R6) (R11 \ R12 + A \ C2 \ R11 \ R12 \ R3 \ s) \end{aligned}$

■ A.5.5 Voltage Transfer Function

```
H = V4/V1 /. CircuitResponse //Together //Simplify;
Ha = Limit[H, A->Infinity];
Print["H(s) = ",
      Collect[Numerator[Ha],s]/Collect[Denominator[Ha],s]]
```

$$H(s) = \frac{(R12 (R5 + R6))}{(R11 R5 + R12 R5 + (C4 R11 R12 R5 + C4 R11 R3 R5 + C4 R12 R3 R5 - C2 R11 R12 R6) s + C2 C4 R11 R12 R3 R5 s^2)}$$

■ A.5.6 Definitions and Procedures

```
PoleQpole[H_,s_] := Module[{den,fp,Qp},
  den = Denominator[H];
  fp = Sqrt[Coefficient[den,s,0]/Coefficient[den,s,2]]/(2*Pi);
  Qp = (Coefficient[den,s,2]/Coefficient[den,s,1])*(2*Pi*fp);
  Simplify[{fp, Qp}]];
ZeroQzero[H_,s_] := Module[{fz,num,Qz0},
  num = Numerator[H];
  Qz0 = (Coefficient[num,s,2]/Coefficient[num,s,1]);
  fz = Sqrt[Coefficient[num,s,0]/Coefficient[num,s,2]]/(2*Pi);
  Simplify[{fz, Qz0*fz}]];
Sensitivity[F_,x_] := (x/F)*D[F,x];
GSP[F_,A_] := Limit[A*Sensitivity[F,A],A->Infinity]//Simplify;
PrintLabeledList[expressions_List,labels_List] := Map[
  Print[#[[1]]," = ",#[[2]]]&
  ,Transpose[{labels,expressions}]
];
```

■ A.5.7 Poles, Zeros, Q-Factors

```
{fp,Qp} = Simplify[PoleQpole[H,s]];
PrintLabeledList[{fp,Qp},{ "fp","Qp"}];
```

$$fp = \frac{\sqrt{\frac{R11 + R12}{C2 C4 R11 R12 R3}}}{2 \text{ Pi}}$$

$$Qp = \frac{(C2 C4 R11 R12 \sqrt{\frac{R11 + R12}{C2 C4 R11 R12 R3}} R3 (R5 + A R5 + R6))}{C2 C4 R11 R12 R3}$$

$$(C2 R11 R12 R5 + C4 R11 R12 R5 + A C4 R11 R12 R5 + C4 R11 R3 R5 + A C4 R11 R3 R5 + C4 R12 R3 R5 + A C4 R12 R3 R5 + C2 R11 R12 R6 - A C2 R11 R12 R6 + C4 R11 R12 R6 + C4 R11 R3 R6 + C4 R12 R3 R6)$$

■ A.5.8 Gain-Sensitivity Product (GSP)

```
GSPfp = GSP[fp,A];
GSPQp = GSP[Qp,A];
PrintLabeledList[{GSPfp,GSPQp},{ "GSPfp", "GSPQp"}];

GSPfp = 0

GSPQp = 
$$\frac{C2 R11 R12 (R5 + R6)^2}{R5 (C4 R11 R12 R5 + C4 R11 R3 R5 + C4 R12 R3 R5 + C2 R11 R12 R6)}$$

```

■ A.5.9 Design

■ Find Element Values

```
DesignLPMQ[K_,Qp_,wp_,P_,C2x_,C4x_,R5x_] := Module[
{C2,C4,R1,R11,R12,R3,R5,R6,Ko},
C2 = C2x;
C4 = C4x;
R1 = 1/(wp*Sqrt[C2x*C4x*P]);
R3 = P*R1;
R5 = R5x;
R6 = R5*((1+P)*C4/C2-Sqrt[P*C4/C2]/Qp);
Ko = 1+R6/R5;
R11 = R1*Ko/K;
R12 = R1*Ko/(Ko-K);
{R11,R12,C2,R3,C4,R5,R6}
];
{R11,R12,C2,R3,C4,R5,R6} = Together[DesignLPMQ[K,Q,W,P,C2x,C4x,R5x]];
```

■ A.5.10 Design Example

```
values = {K -> 1., Q -> 7.5, W -> 2*Pi*2500., P -> 1.5333078
, C2x -> 33.*10^(-9), C4x -> 10.*10^(-9), R5x -> 6800.} //N;
PrintLabeledList[N[{K,Q,W/(2*Pi),P} /. values]
,{"K","Qp","fp (Hz)","P"} ];
Print["-----"]
PrintLabeledList[Together[{R11,R12,C2*10^9,R3,C4*10^9,R5,R6} /. values],
{"R11 (ohm)","R12 (ohm)","C2 (nF)","R3 (ohm)","C4 (nF)","R5 (ohm)","R6 (ohm)"}];

K = 1.
Qp = 7.5
fp (Hz) = 2500.
P = 1.53331
-----
R11 (ohm) = 4745.54
R12 (ohm) = 7011.9
C2 (nF) = 33.
R3 (ohm) = 4339.48
C4 (nF) = 10.
R5 (ohm) = 6800.
R6 (ohm) = 4602.13
```

■ A.5.11 Optimization


■ Find P for Low Gain-Sensitivity Product

```
values = {K -> 1.476288, Q -> 7.5, W -> 2*Pi*2500.,
, C2x -> 100.*10^(-9), C4x -> 15.*10^(-9), R5x -> 10000.} //N;
gspQp = Together[Simplify[GSPQp] /. values]
```

$$0.435711 (7.66667 - 0.344265 \sqrt{P} + 1. P)^2$$

$$\sqrt{P}$$
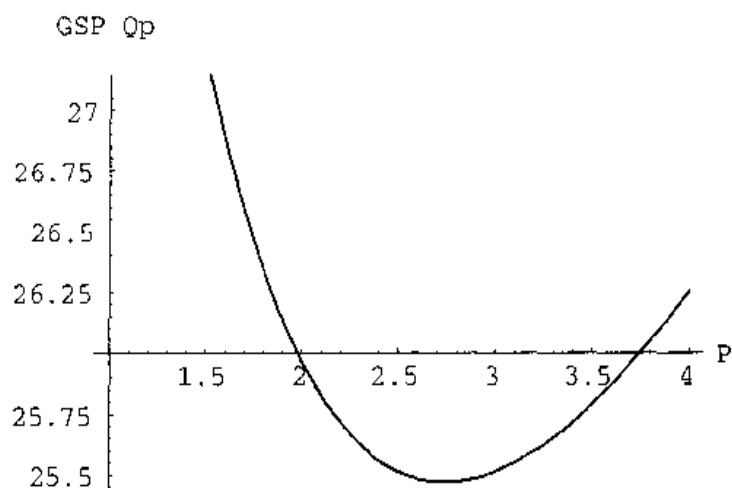
```
P1 = 1.;
P2 = 4.;
Plot[gspQp /. values
, {P, P1, P2}
, AxesLabel -> {"P", "GSP Qp"}
];
```



```
{GSPmin,Pset} = FindMinimum[gspQp,{P,P1,P2}]
```

```
{25.4701, {P -> 2.74571}}
```

```
PrintLabeledList[N[{K,Q,W/(2*Pi),P} /. values /.Pset]
```

```
, {"K", "Qp", "fp (Hz)", "P"} ];
```

```
Print["-----"]
```

```
PrintLabeledList[Together[{R11,R12,C2*10^9,R3,C4*10^9,R5,R6} /. values /.Pset],
```

```
{"R11 (ohm)", "R12 (ohm)", "C2 (nF)", "R3 (ohm)", "C4 (nF)", "R5 (ohm)", "R6 (ohm)"}]
```

```
K = 1.47629
```

```
Qp = 7.5
```

```
fp (Hz) = 2500.
```

```
P = 2.74571
```

```
-----
R11 (ohm) = 991.99
```

```

9
R12 (ohm) = 1.81368 10
C2 (nF) = 100.
R3 (ohm) = 2723.72
C4 (nF) = 15.
R5 (ohm) = 10000.
R6 (ohm) = 4762.89

Hhpmq = Together[Ha /. Pset /. values] ;
num = Numerator[Hhpmq];
den = Denominator[Hhpmq];
numlist = CoefficientList[num,s];
denlist = CoefficientList[den,s];
Hhpmq = (1/denlist[[3]]) * num/(den/denlist[[3]])//Factor


```

```

8
3.64259 10
-----
8      2
2.4674 10 + 2094.4 s + 1. s

Plot[{Abs[Hhpmq] /. s -> N[I*2*Pi*f]}
, {f, 100, 10000}
, PlotRange -> All
, Ticks -> {{0,2000,5000,10000},{0,2,4,6,8,10}}
, AxesLabel -> {"f (Hz)", "M(f)"}];

```

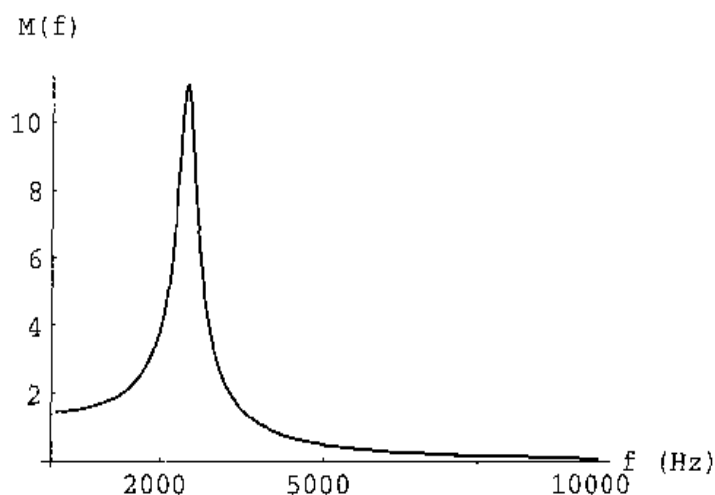

■ Remark

We choose $P=2.7457$ as a good choice because we obtain small GSP and $1/R_{12} \approx 0$.

A.6 General Purpose High-Q-Factor RC Filter Analysis and Design

Miroslav D. Lutovac, Dejan V. Tasic and Brian L. Evans

lutovac@iritel.bg.ac.yu tasic@galeb.etf.bg.ac.yu bevans@ece.utexas.edu

■ A.6.1 References


1. G. S. Moschytz and P. Horn,
Active Filter Design Handbook
For Use with Programmable Pocket Calculators and Mini Computers
John Wiley and Sons, Ltd., New York, 1981 pp. 64–65.
2. W. J. Kerwin, L. P. Huelsman, and R. W. Newcomb,
State-variable synthesis for insensitive integrated circuit transfer functions,
IEEE J. Solid-State Circuits, SC-2, pp. 87–92, September, 1967.
3. D.V. Tasic, M.D. Lutovac, B.L. Evans, I.M. Markoski,
“A tool for symbolic analysis and design of analog active filters,”
5th Int. Workshop, Symbolic Methods, Applications, Circuit Design,
SMACD'98, Kaiserslautern, Germany, pp. 71–74, Oct. 1998.
4. M. D. Lutovac, D. V. Tasic and B. L. Evans,
“Advanced Filter Design for Signal Processing using MATLAB and Mathematica,”
<http://iritel.iritel.bg.ac.yu/~lutovac/www/afdhome.htm>
<http://galeb.etf.bg.ac.yu/~tasic/afdhome.htm>
<http://www.ece.utexas.edu/~bevans/>

■ A.6.2 Initialization

```
SetDirectory[HomeDirectory[]];
<<afd\math\m\clearall.m
<<afd\math\m\drawafil.m
<<afd\math\m\drawarc.m
```

■ A.6.3 Schematic

```
DrawGPHQ[0,0,1/2,1/0.8];
```

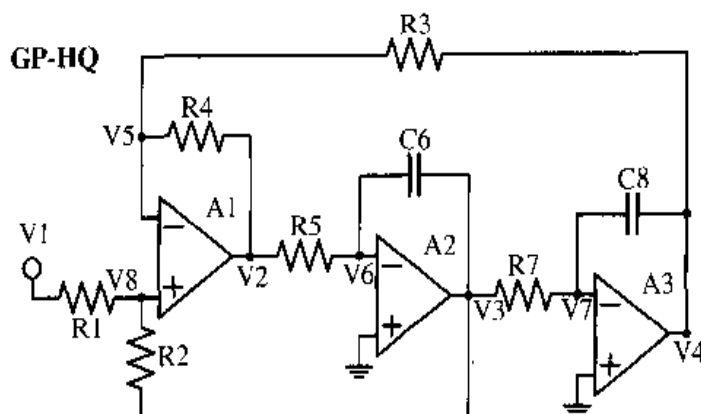

■ A.6.4 Circuit Analysis

■ Reduced Modified Nodal Analysis

```
CircuitEquations = {V1 == Vg
, V2 == A*(V8 - V5)
, V3 == -A*V6
, V4 == -A*V7
, (V5-V2)/R4 + (V5-V4)/R3 == 0
, (V6-V2)/R5 + (V6-V3)/(1/(s*C6)) ==0
, (V7-V3)/R7 + (V7-V4)/(1/(s*C8)) ==0
, (V8-V1)/R1 + (V8-V3)/R2 ==0};
NodeVoltages = {V1,V2,V3,V4,V5,V6,V7,V8};
CircuitResponse = Together[Flatten[
  Solve[CircuitEquations,NodeVoltages]
]];

```

■ A.6.5 Voltage Transfer Function

```
H = V4/V1 /. CircuitResponse //Together //Simplify;
Ha = Limit[H, A->Infinity];
Print["H(s) = ",
  Collect[Numerator[Ha],s]/Collect[Denominator[Ha],s]]

```

$$H(s) = \frac{R_2 (R_3 + R_4)}{(R_1 R_4 + R_2 R_4 + (C_8 R_1 R_3 R_7 + C_8 R_1 R_4 R_7) s + (C_6 C_8 R_1 R_3 R_5 R_7 + C_6 C_8 R_2 R_3 R_5 R_7) s^2)}$$

```
Klp = Factor[Ha /. s->0]

```

$$\frac{R_2 (R_3 + R_4)}{(R_1 + R_2) R_4}$$

```
Hh = V2/V1 /. CircuitResponse //Together //Simplify;
Hha = Limit[Hh, A->Infinity];
Print["Hh(s) = ",
  Collect[Numerator[Hha],s]/Collect[Denominator[Hha],s]]

```

$$Hh(s) = \frac{(C_6 C_8 R_2 (R_3 + R_4) R_5 R_7 s^2)}{(R_1 R_4 + R_2 R_4 + (C_8 R_1 R_3 R_7 + C_8 R_1 R_4 R_7) s + (C_6 C_8 R_1 R_3 R_5 R_7 + C_6 C_8 R_2 R_3 R_5 R_7) s^2)}$$

```
Khp = Factor[Limit[Hha , s->Infinity]]

```

$$\frac{R_2 (R_3 + R_4)}{(R_1 + R_2) R_3}$$

```
Hb = V3/V1 /. CircuitResponse //Together //Simplify;
Hba = Limit[Hb, A->Infinity];
Print["Hb(s) = ",
Collect[Numerator[Hba],s]/Collect[Denominator[Hba],s]]
```

$$H_b(s) = -\frac{(C_8 R_2 (R_3 + R_4) R_7 s)}{(R_1 R_4 + R_2 R_4 + (C_8 R_1 R_3 R_7 + C_8 R_1 R_4 R_7) s + (C_6 C_8 R_1 R_3 R_5 R_7 + C_6 C_8 R_2 R_3 R_5 R_7) s^2)}$$

```
num = Numerator[Hba];
den = Denominator[Hba];
numlist = CoefficientList[num,s];
denlist = CoefficientList[den,s];
Hbp = Factor[numlist[[2]]/denlist[[2]]]
```

$$-\frac{R_2}{R_1}$$

■ A.6.6 Definitions and Procedures

```
PoleQpole[H_,s_] := Module[{den,fp,Qp},
den = Denominator[H];
fp = Sqrt[Coefficient[den,s,0]/Coefficient[den,s,2]]/(2*Pi);
Qp = (Coefficient[den,s,2]/Coefficient[den,s,1])*(2*Pi*fp);
Simplify[{fp, Qp}];
ZeroQzero[H_,s_] := Module[{fz,num,Qz0},
num = Numerator[H];
Qz0 = (Coefficient[num,s,2]/Coefficient[num,s,1]);
fz = Sqrt[Coefficient[num,s,0]/Coefficient[num,s,2]]/(2*Pi);
Simplify[{fz, Qz0*fz}];
Sensitivity[F_,x_] := (x/F)*D[F,x];
GSP[F_,A_] := Limit[A*Sensitivity[F,A],A->Infinity]//Simplify;
GSPepsA[F_,epsA_] := -(1/epsA)*Sensitivity[F,epsA]//Together;
PrintLabeledList[expressions.List,labels.List] := Map[
Print[#[[1]]," = ",#[[2]]]&
,Transpose[{labels,expressions}]
];
```

■ A.6.7 Poles, Zeros, Q-Factors

```
{fp,Qp} = Simplify[PoleQpole[H,s]];
fp0 = Together[Limit[fp,A-> Infinity]];
Qp0 = Limit[Qp,A-> Infinity];
PrintLabeledList[{fp0,Qp0},{ "fp","Qp"}];
```


$$fp = \frac{\sqrt{\frac{R4}{C6 C8 R3 R5 R7}}}{2 \text{ Pi}}$$

$$Qp = \frac{C6 (R1 + R2) R3 R5 \sqrt{\frac{R4}{C6 C8 R3 R5 R7}}}{R1 (R3 + R4)}$$

■ A.6.8 Gain-Sensitivity Product (GSP)

```
fpepsA = Together[fp /. A->1/e];
QpepsA = Together[Qp /. A->1/e];
GSPQp = Simplify[GSPepsA[QpepsA,e] /. e->0];
GSPfp = Simplify[GSPepsA[fpepsA,e] /. e->0];
PrintLabeledList[{GSPfp,GSPQp},{ "GSPfp", "GSPQp"}];
```

$$GSPfp = \frac{-(R1 R3)^2 + 2 R1 R3 R4 + 3 R2 R3 R4 + R1 R4^2 + R2 R4^2}{2 R3 (R1 R4 + R2 R4)}$$

$$GSPQp = \frac{(2 C6 R1^2 R3 R4 R5 + 4 C6 R1 R2 R3 R4 R5 + 2 C6 R2^2 R3 R4 R5 - C8 R1^2 R3 R7 - C8 R1^2 R3 R4 R7 + 3 C8 R1 R2 R3 R4 R7 + 2 C8 R2^2 R3 R4 R7 - 3 C8 R1^2 R3 R4 R7 - 2 C8 R1 R2 R3 R4 R7 - C8 R1^2 R4 R7 - C8 R1 R2 R4 R7) / (2 R3 (R1 R4 + R2 R4) (C8 R1 R3 R7 + C8 R1 R4 R7))}{1}$$

■ A.6.9 Design

■ Find Element Values

```
DesignGPHQ[Qp_,wp_,Cx_,Rx_] :=
Module[{C6,C8,R1,R2,R3,R4,R5,R7,Ro},
C6 = Cx;
C8 = Cx;
Ro = 1/(wp*Cx);
R1 = Rx;
R3 = Rx;
R5 = Rx;
R7 = Rx;
R4 = Rx*(Rx/Ro)^2;
R2 = Rx*(Qp*(1+R4/Rx)/Sqrt[R4/Rx]-1);
{R1,R2,R3,R4,R5,C6,R7,C8};
{R1,R2,R3,R4,R5,C6,R7,C8} = DesignGPHQ[Q,Wp,Co,Rd];
```

■ Design Examples

```
values = {Q -> 6., Wp -> 2*Pi*1500.
, Co -> 68.*10^(-9), Rd -> 1800.} //N;
gspQpfp = Together[Abs[GSPQp/2]+Abs[Q*GSPfp] /. values];
```

```
PrintLabeledList[N[{Q,Wp/(2*Pi),gspQpfp} /. values]
,{"Qp","fp (Hz)","GSP"}];
Print["-----"]
PrintLabeledList[Together[{R1,R2,R3,R4,R5,C6*10^9,R7,C8*10^9} /. values]
,{"R1 (ohm)","R2 (ohm)","R3 (ohm)","R4 (ohm)","R5 (ohm)","C6 (nF)"
,"R7 (ohm)","C8 (nF)"}];

Qp = 6.
fp (Hz) = 1500.
GSP = 17.1412
-----
R1 (ohm) = 1800.
R2 (ohm) = 20020.9
R3 (ohm) = 1800.
R4 (ohm) = 2395.4
R5 (ohm) = 1800.
C6 (nF) = 68.
R7 (ohm) = 1800.
C8 (nF) = 68.

values = {Q -> 25., Wp -> 2*Pi*1500.
, Co -> 22.*10^(-9), Rd -> 4700.} //N;
gspQpfp = Together[Abs[GSPQp/2]+Abs[Q*GSPfp] /. values];
PrintLabeledList[N[{Q,Wp/(2*Pi),gspQpfp} /. values]
,{"Qp","fp (Hz)","GSP"}];
Print["-----"]
PrintLabeledList[Together[{R1,R2,R3,R4,R5,C6*10^9,R7,C8*10^9} /. values]
,{"R1 (ohm)","R2 (ohm)","R3 (ohm)","R4 (ohm)","R5 (ohm)","C6 (nF)"
,"R7 (ohm)","C8 (nF)"}];


Qp = 25.
fp (Hz) = 1500.
GSP = 74.014
-----
R1 (ohm) = 4700.
R2 (ohm) = 230378.
R3 (ohm) = 4700.
R4 (ohm) = 4463.56
R5 (ohm) = 4700.
C6 (nF) = 22.
R7 (ohm) = 4700.
C8 (nF) = 22.
```

■ A.6.10 Optimization

■ Find Rd for Low Gain-Sensitivity Product

```
values = {Q -> 25., Wp -> 2*Pi*1500.
, Co -> 22.*10^(-9)} //N;
gspQpfp1 = Together[Abs[GSPQp/2.] + Abs[Q*GSPfp] /. values] //Simplify;
```
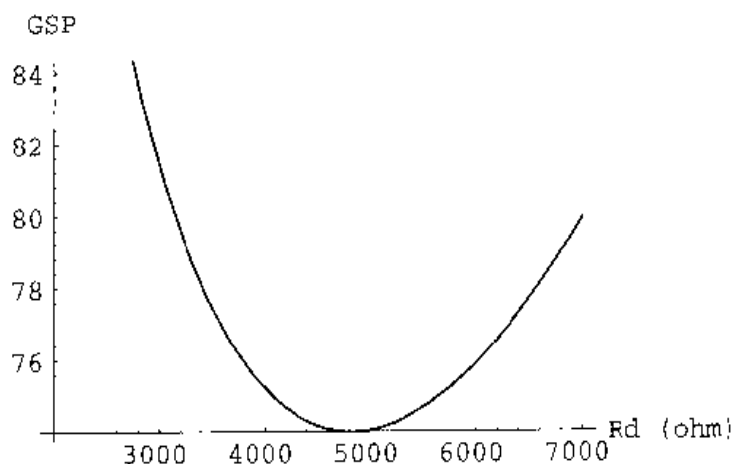
```
r1 = 2000;
r2 = 7000;
Plot[{gspQpfp1}
, {Rd, r1, r2}
, AxesLabel -> {"Rd (ohm)", "GSP"}
];
```



```
{Gspmin, Rset} = FindMinimum[gspQpfp1, {Rd, r1, r2}]

{73.99, {Rd -> 4822.22}}

values = {Q -> 25., Wp -> 2*Pi*1500.
, Co -> 22.*10^(-9)} /. N;
gspQpfp = Together[Abs[GSPQp/2]+Abs[Q*GSPfp] /. values /. Rset];
PrintLabeledList[N[{Q, Wp/(2*Pi), gspQpfp} /. values /. Rset]
, {"Qp", "fp (Hz)", "GSP"} ];
Print["-----"]
PrintLabeledList[Together[{R1, R2, R3, R4, R5, C6*10^9, R7, C8*10^9} /. values /. Rset]
, {"R1 (ohm)", "R2 (ohm)", "R3 (ohm)", "R4 (ohm)", "R5 (ohm)", "C6 (nF)"
, "R7 (ohm)", "C8 (nF)"}];

Qp = 25.
fp (Hz) = 1500.
GSP = 73.99

-----
R1 (ohm) = 4822.22
R2 (ohm) = 236289.
R3 (ohm) = 4822.22
R4 (ohm) = 4820.9
R5 (ohm) = 4822.22
C6 (nF) = 22.
R7 (ohm) = 4822.22
C8 (nF) = 22.
```

668 App. A Example *Mathematica* Notebooks

```
Hlp = Hla /. values /. Rset//Together;
num = Numerator[Hlp];
den = Denominator[Hlp];
numlist = CoefficientList[num,s];
denlist = CoefficientList[den,s];
Hlp = 1/denlist[[3]] * num/(den/denlist[[3]])//Factor
```

$$\frac{1.74124 \times 10^8}{8.88264 \times 10^7 + 376.991 s + 1. s^2}$$


```
Hhp = Hha /. values /. Rset//Together;
num = Numerator[Hhp];
den = Denominator[Hhp];
numlist = CoefficientList[num,s];
denlist = CoefficientList[den,s];
Hhp = 1/denlist[[3]] * num/(den/denlist[[3]])//Factor
```

$$\frac{1.95973 s^2}{8.88264 \times 10^7 + 376.991 s + 1. s^2}$$

```
Hbp = Hba /. values /. Rset//Together;
num = Numerator[Hbp];
den = Denominator[Hbp];
numlist = CoefficientList[num,s];
denlist = CoefficientList[den,s];
Hbp = 1/denlist[[3]] * num/(den/denlist[[3]])//Factor
```

$$\frac{-18472.6 s}{8.88264 \times 10^7 + 376.991 s + 1. s^2}$$
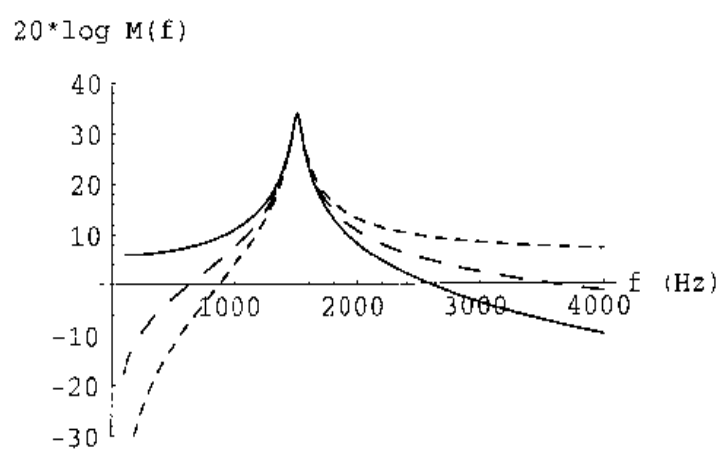
```
AHlp = 20*Log[10,Abs[Hlp]] /. s -> N[I*2*Pi*f];
AHhp = 20*Log[10,Abs[Hhp]] /. s -> N[I*2*Pi*f];
AHbp = 20*Log[10,Abs[Hbp]] /. s -> N[I*2*Pi*f];
Plot[{AHlp, AHhp, AHbp}
, {f, 100, 4000}
, PlotRange -> {-30,40}
, PlotStyle -> {Dashing[{}],
Dashing[.02],
Dashing[.04]}
, AxesLabel -> {"f (Hz)", "20*log M(f)"}
];
```



A.7 Advanced Analog Filter Design Case Studies

Miroslav D. Lutovac, Dejan V. Tasic and Brian L. Evans

lutovac@iritel.bg.ac.yu tasic@galeb.etf.bg.ac.yu bevans@ece.utexas.edu

■ A.7.1 References

1. D.V. Tasic, M.D.Lutovac, B.L.Evans,
"Advanced filter design,"
Proc. IEEE Asilomar Conf. Signal, Systems, Computer,
Nov. 1997, pp.710–715.
2. M. D. Lutovac, D. V. Tasic and B. L. Evans,
"Advanced Filter Design for Signal Processing using MATLAB and Mathematica,"
<http://iritel.iritel.bg.ac.yu/lutovac/www/afdhome.htm>
<http://galeb.etf.bg.ac.yu/tasic/afdhome.htm>
<http://www.ece.utexas.edu/~bevans/>

■ A.7.2 Initialization

```
SetDirectory[HomeDirectory[]];
<<afd\math\m\clearall.m
<<graphics\graphics'
```

■ A.7.3 Notation

a – selectivity factor
 a_p – maximum passband loss, dB, of realized filter
 A_p – maximum passband loss, dB, in specification
 a_s – minimum stopband loss, dB, of realized filter
 A_s – minimum stopband loss, dB, in specification
 $A_{2a}(n, A_p, A_s)$ – minimum selectivity factor from attenuation spec
 $A_{2K}(A)$ – characteristic function in terms of attenuation in dB
 e – ripple factor
 f_p – passband edge [Hz] of realized filter
 F_p – passband edge [Hz] in specification
 f_s – stopband edge [Hz] of realized filter
 F_s – stopband edge [Hz] in specification
 $Ke(n, a, e, x)$ – characteristic function
 $L(n, a)$ – discrimination factor
 n – order
 $n_{but}(F_p, F_s, A_p, A_s)$ minimum Butterworth order from specification
 $n_{cheb}(F_p, F_s, A_p, A_s)$ minimum Chebyshev order from specification
 $n_{ellip}(F_p, F_s, A_p, A_s)$ minimum order from specification
 $q(k)$ – modular constant
 $R(n, a, x)$ – elliptic rational function
 $S(n, a, e)$ – list of transfer function poles
 $S(n, a, e, i)$ – transfer function pole

SA – attenuation specification
 SK – characteristic function specification
 X(n,a) – list of zeros of elliptic rational function
 X(n,a,i) – zero of elliptic rational function
 Z(n,a,e) – zeta function

■ A.7.4 Definitions and Procedures

```
X[n_Integer,a_,i_Integer] := -JacobiCD[
  (2*i-1)*EllipticK[1/a^2]/n, 1/a^2
];
X[n_Integer,a_,i_Integer] := 0 /; And[i==(n+1)/2,OddQ[n]];
X[n_Integer,a_] := X[n,a,#]& /@ Range[n];
L[n_Integer,a_] := Block[{i,r},
  If[EvenQ[n],
    r = (1/a^n)*Product[(a^2 - X[n,a,i]^2)^2, {i,n/2}]/
      Product[(1 - X[n,a,i]^2)^2, {i,n/2}];,
    r = (1/a^(n-2))*Product[(a^2 - X[n,a,i]^2)^2, {i,(n-1)/2}]/
      Product[(1 - X[n,a,i]^2)^2, {i,(n-1)/2}];
  ];
  r
];
R[n_Integer,a_,x_] := Block[{i,r,r0},
  If[EvenQ[n],
    r = Product[x^2 - X[n,a,i]^2, {i,n/2}]/
      Product[x^2 - a^2/X[n,a,i]^2, {i,n/2}];
    r0 = Product[1 - X[n,a,i]^2, {i,n/2}]/
      Product[1 - a^2/X[n,a,i]^2, {i,n/2}];,
    r = x*Product[x^2 - X[n,a,i]^2, {i,(n-1)/2}]/
      Product[x^2 - a^2/X[n,a,i]^2, {i,(n-1)/2}];
    r0 = Product[1 - X[n,a,i]^2, {i,(n-1)/2}]/
      Product[1 - a^2/X[n,a,i]^2, {i,(n-1)/2}];
  ];
  r/r0
];
Z[n_Integer,a_,e_] := JacobiSN[
  InverseJacobiSN[1/Sqrt[1+e^2],1-1/(L[n,a])^2]*
  EllipticK[1-1/a^2]/EllipticK[1-1/(L[n,a])^2],1-1/a^2
];
S[n_Integer,a_,e_,i_Integer] := Block[
{den,num,numim,numre,x,z},
  x = X[n,a,i];
  z = Z[n,a,e];
  numre = -z*Sqrt[1 - z^2]*Sqrt[1 - x^2]*Sqrt[1 - x^2/a^2];
  numim = x*Sqrt[1 - (1-1/a^2)*z^2];
  num = numre + I*numim;
```

672 App. A Example *Mathematica* Notebooks

```
den = 1 - (1 - x^2/a^2)*z^2;
num/den
];
S[n_Integer, a_, e_] := S[n,a,e,#]& /@ Range[n];
A2K[A_] := Sqrt[1 - 10^(-A/10)]/10^(-A/20);
Ke[n_Integer, a_, e_, x_] := e*Abs[R[n,a,x]];
```

■ A.7.5 Specification

```
SA = {3000., 3225., 0.2, 40.};
{Fp, Fs, Ap, As} = SA;
Kp = A2K[Ap];
Ks = A2K[As];
SK = {Fp, Fs, Kp, Ks}

{3000., 3225., 0.217091, 99.995}
```

■ A.7.6 Minimum Order

```
nellip[Fp_,Fs_,Ap_,As_] := Block[
  {num, den,
   k = Fp/Fs,
   L = Sqrt[(-1 + 10^(As/10))/(-1 + 10^(Ap/10))]},
  num = EllipticK[1-1/L^2]/EllipticK[1/L^2];
  den = EllipticK[1-k^2]/EllipticK[k^2];
  Ceiling[num/den//N]
];
ncheb[Fp_,Fs_,Ap_,As_] := Block[
  {L = Sqrt[(-1 + 10^(As/10))/(-1 + 10^(Ap/10))],
   aspec = Fs/Fp},
  Ceiling[ArcCosh[L]/ArcCosh[aspec]//N]
];
nbut[Fp_,Fs_,Ap_,As_] := Block[
  {L = Sqrt[(-1 + 10^(As/10))/(-1 + 10^(Ap/10))],
   aspec = Fs/Fp},
  Ceiling[Log[10,L]/Log[10,aspec]//N]
];
{nellip[Fp,Fs,Ap,As], ncheb[Fp,Fs,Ap,As], nbut[Fp,Fs,Ap,As]}
nmin = nellip[Fp,Fs,Ap,As];
nmax = 2*nmin;
nlist = Range[nmin,nmax]

{8, 18, 85}
{8, 9, 10, 11, 12, 13, 14, 15, 16}
```


■ A.7.7 Range of Selectivity Factor and Ripple Factor

```

q[k_] := Block[{c,e,r,s,t},
  If[k<=1/Sqrt[2.0],
    t = (1/2)*(1 - (1-k^2)^(1/4))/(1 + (1-k^2)^(1/4));,
    t = (1/2)*(1 - Sqrt[k])/(1 + Sqrt[k]);
  ];
  e = {1,5, 9, 13, 17, 21, 25, 29, 33, 37};
  c = {1,2,15,150,1707,20910,268616,3567400,48555069,673458874};
  s = Sum[c[[i]]*(t^e[[i]]),{i,Length[e]}];
  If[k<=1/Sqrt[2.0],
    r = s;,
    r = Exp[Pi^2/Log[s]];
  ];
  N[r]
];

A2a[n_,Ap_,As_] := Block[
  {m, num, den, terms=9, L, qL},
  L = Sqrt[(-1 + 10^(As/10))/(-1 + 10^(Ap/10))];
  qL = q[1/L]^(1/n);
  num = 1 + 2*Sum[(-1)^m*(qL)^(m^2), {m,1,terms}];
  den = 1 + 2*Sum[(qL)^(m^2), {m,1,terms}];
  1/Sqrt[1 - (num/den)^4]
];

amin8 = A2a[nmin,Ap,As];
amax8 = a/. FindRoot[R[nmin,a,Fs/Fp]==Ks/Kp, {a,Fs/Fp,1.1}];
amin9 = A2a[9,Ap,As];
amax9 = a/. FindRoot[R[9,a,Fs/Fp]==Ks/Kp, {a,amax8,1.1}];
amin10 = A2a[10,Ap,As];
amax10 = a/. FindRoot[R[10,a,Fs/Fp]==Ks/Kp, {a,amax9,1.2}];
amin11 = A2a[11,Ap,As];
amax11 = a/. FindRoot[R[11,a,Fs/Fp]==Ks/Kp, {a,amax10,1.2}];
amin12 = A2a[12,Ap,As];
amax12 = a/. FindRoot[R[12,a,Fs/Fp]==Ks/Kp, {a,amax11,1.2}];
amin13 = A2a[13,Ap,As];
amax13 = a/. FindRoot[R[13,a,Fs/Fp]==Ks/Kp, {a,amax12,1.3}];
amin14 = A2a[14,Ap,As];
amax14 = a/. FindRoot[R[14,a,Fs/Fp]==Ks/Kp, {a,amax13,1.4}];
amin15 = A2a[15,Ap,As];
amax15 = a/. FindRoot[R[15,a,Fs/Fp]==Ks/Kp, {a,amax14,1.6}];
amin16 = A2a[16,Ap,As];
amax16 = a/. FindRoot[R[16,a,Fs/Fp]==Ks/Kp, {a,amax15,1.9}];
aminlist = {amin8,amin9,amin10,amin11,amin12,amin13,amin14,amin15,amin16};
amaxlist = {amax8,amax9,amax10,amax11,amax12,amax13,amax14,amax15,amax16};
eminlist = Table[Ks/L[n,amaxlist[[n-8+1]]], {n,nmin,nmax}];
{emin8,emin9,emin10,emin11,emin12,emin13,emin14,emin15,emin16} = eminlist;
emax = Kp;
emaxlist = Table[Kp,{nmax-nmin+1}];

```

```
TableForm[Transpose[{nlist, aminlist, amaxlist, eminlist, emaxlist}]
, TableHeadings->{{}, {"n", "amin", "amax", "emin", "emax"}}]
```

n	amin	amax	emin	emax
8	1.04285	1.08323	0.0757872	0.217091
9	1.022	1.09807	0.0184689	0.217091
10	1.01135	1.12013	0.00368669	0.217091
11	1.00587	1.15172	0.000578651	0.217091
12	1.00304	1.19663	0.0000676012	0.217091
			-6	
13	1.00158	1.26158	5.39161 10	0.217091
			-7	
14	1.00082	1.35951	2.53319 10	0.217091
			-9	
15	1.00042	1.51914	5.28479 10	0.217091
			-11	
16	1.00022	1.82219	2.51893 10	0.217091


■ A.7.8 Range of Edge Frequencies

```
fpminlist = Fs / amaxlist;
{fpmin8, fpmin9, fpmin10, fpmin11, fpmin12, fpmin13,
 fpmin14, fpmin15, fpmin16} = fpminlist;
fpmaxlist = Fs / aminlist;
{fpmax8, fpmax9, fpmax10, fpmax11, fpmax12, fpmax13,
 fpmax14, fpmax15, fpmax16} = fpmaxlist;
fsminlist = Fp * aminlist;
{fsmin8, fsmin9, fsmin10, fsmin11, fsmin12, fsmin13,
 fsmin14, fsmin15, fsmin16} = fsminlist;
fsmaxlist = Fp * amaxlist;
{fsmax8, fsmax9, fsmax10, fsmax11, fsmax12, fsmax13,
 fsmax14, fsmax15, fsmax16} = fsmaxlist;
TableForm[Transpose[{nlist, fpminlist, fpmaxlist, fsminlist, fsmaxlist}]
, TableHeadings->{{}, {"n", "fpmin", "fpmax", "fsmin", "fsmax (Hz)"}]}
```


n	fpmin	fpmax	fsmin	fsmax (Hz)
8	2977.2	3092.49	3128.55	3249.7
9	2936.97	3155.57	3066.01	3294.21
10	2879.14	3188.79	3034.06	3360.38
11	2800.16	3206.17	3017.62	3455.16
12	2695.06	3215.22	3009.13	3589.89
13	2556.32	3219.92	3004.73	3784.74
14	2372.18	3222.36	3002.45	4078.53
15	2122.91	3223.63	3001.27	4557.42
16	1769.85	3224.29	3000.66	5466.56

■ A.7.9 Design D1
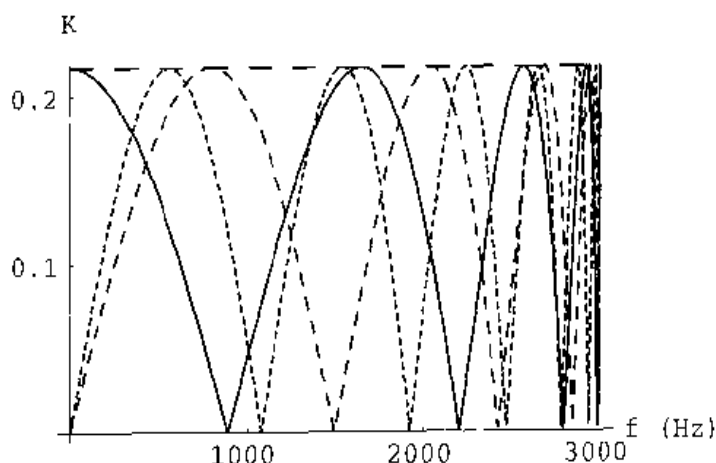
```
Plot[Evaluate[{Kp
    , Ke[ 8, Fs/Fp, emax, f/Fp]
    , Ke[ 9, Fs/Fp, emax, f/Fp]
    , Ke[13, Fs/Fp, emax, f/Fp]
}], {f, 0, Fp}
, AxesLabel -> {"f (Hz)", "K"}
, PlotStyle -> {Dashing[{0.04}],
    Dashing[{}],
    Dashing[{0.02}],
    Dashing[{0.01]}
}
, Ticks -> {{1000, 2000, 3000}, {0, 0.1, 0.2}}
, PlotRange -> All];
```



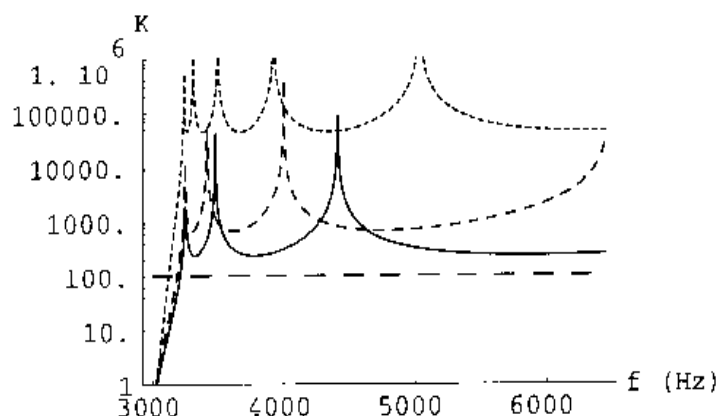
```
LogPlot[Evaluate[{Ks
    , Ke[ 8, Fs/Fp, emax, f/Fp]
    , Ke[ 9, Fs/Fp, emax, f/Fp]
    , Ke[13, Fs/Fp, emax, f/Fp]
}], {f, Fp, 2*Fs}
, AxesLabel -> {"f (Hz)", "K"}
, PlotStyle -> {Dashing[{0.04}],
    Dashing[{}],
    Dashing[{0.02}],
    Dashing[{0.01]}
}
, Ticks -> {{3000, 4000, 5000, 6000}, Automatic}
, PlotRange -> {1, 10^6}];
```




■ A.7.10 Design D2
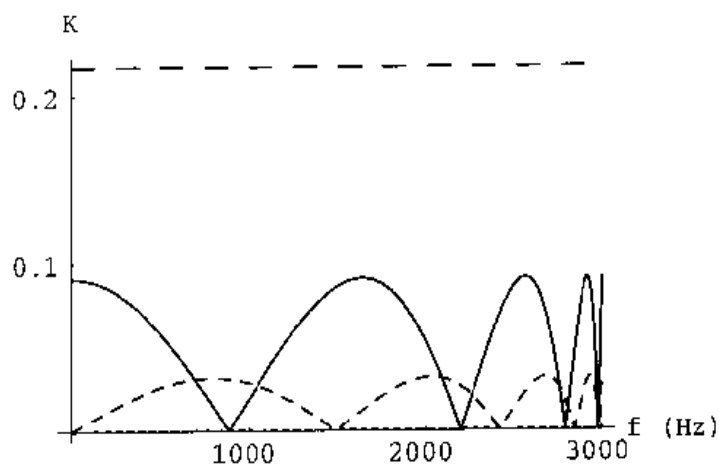
```
Plot[Evaluate[{Kp
  , Ke[ 8, Fs/Fp, Ks/L[ 8,Fs/Fp], f/Fp]
  , Ke[ 9, Fs/Fp, Ks/L[ 9,Fs/Fp], f/Fp]
  , Ke[13, Fs/Fp, Ks/L[13,Fs/Fp], f/Fp]
}], {f,0,Fp}
, AxesLabel -> {"f (Hz)", "K"}
, PlotStyle -> {Dashing[{0.04}],
  Dashing[{}],
  Dashing[{0.02}],
  Dashing[{0.01}]
}
, Ticks -> {{1000, 2000, 3000}, {0, 0.1, 0.2}}
, PlotRange -> All];
```




```
LogPlot[Evaluate[{Ks
  , Ke[ 8, Fs/Fp, Ks/L[ 8,Fs/Fp], f/Fp]
  , Ke[ 9, Fs/Fp, Ks/L[ 9,Fs/Fp], f/Fp]
  , Ke[13, Fs/Fp, Ks/L[13,Fs/Fp], f/Fp]
}], {f,Fp,2*Fs}
```
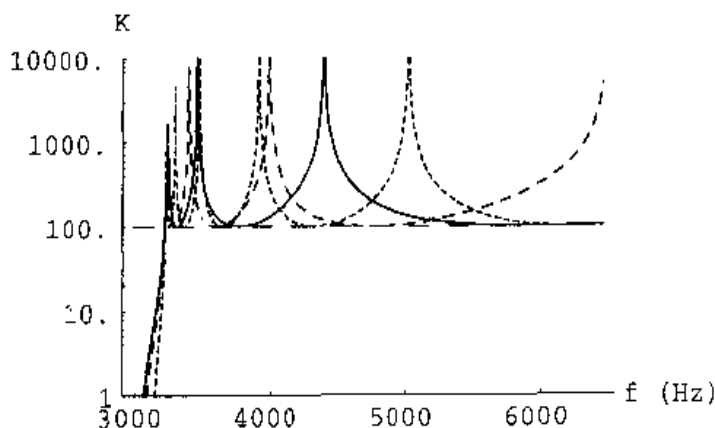
```
, AxesLabel -> {"f (Hz)", "K"}
, PlotStyle -> {Dashing[{0.04}],
                Dashing[{}],
                Dashing[{0.02}],
                Dashing[{0.01}]
            }
, Ticks -> {{3000, 4000, 5000, 6000}, Automatic}
, PlotRange -> {1, 10^4};
```




■ A.7.11 Design D3a

```
Plot[Evaluate[{Kp
                , Ke[ 8, amin8,  emax, f/Fp]
                , Ke[ 9, amin9,  emax, f/Fp]
                , Ke[13, amin13, emax, f/Fp]
            }],
    {f, 0, Fp}
, AxesLabel -> {"f (Hz)", "K"}
, PlotStyle -> {Dashing[{0.04}],
                Dashing[{}],
                Dashing[{0.02}],
                Dashing[{0.01}]
            }
, Ticks -> {{1000, 2000, 3000}, {0, 0.1, 0.2}}
, PlotRange -> All];
```

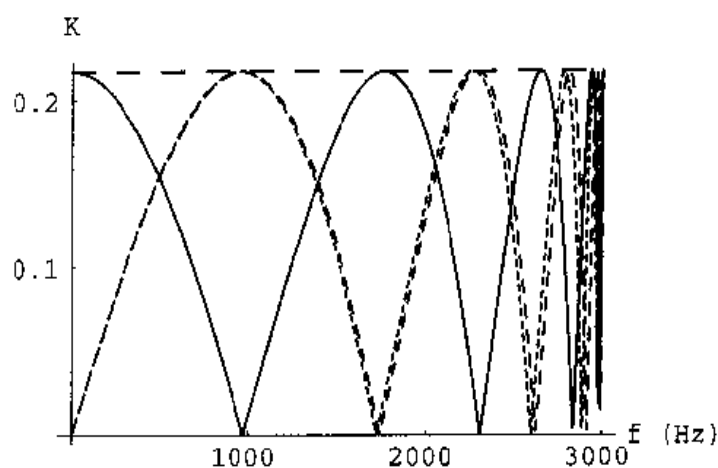

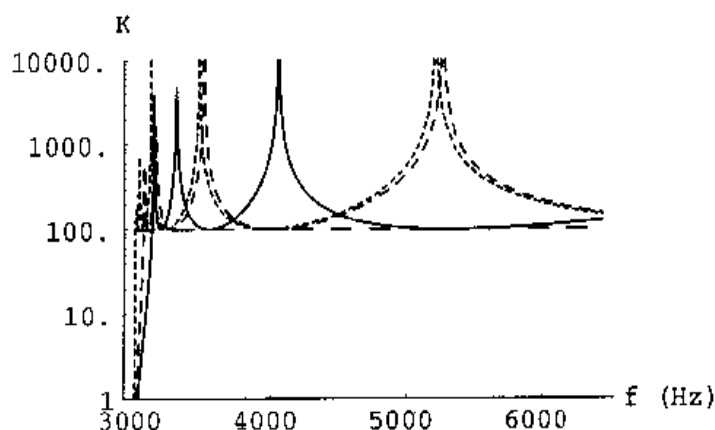
```
LogPlot[Evaluate[{Ks
    , Ke[ 8, amin8,  emax, f/Fp]
    , Ke[ 9, amin9,  emax, f/Fp]
    , Ke[13, amin13, emax, f/Fp]
}], {f, Fp, 2*Fs}
, AxesLabel -> {"f (Hz)", "K"}
, PlotStyle -> {Dashing[{0.04}],
    Dashing[{}],
    Dashing[{0.02}],
    Dashing[{0.01}]
}
, Ticks -> {{3000, 4000, 5000, 6000}, Automatic}
, PlotRange -> {1, 10^4}];
```




```
LogPlot[Evaluate[{Kp, Ks
    , Ke[ 8, amin8,  emax, f/Fp]
    , Ke[ 9, amin9,  emax, f/Fp]
    , Ke[13, amin13, emax, f/Fp]
}], {f, Fp, Fs}
, AxesLabel -> {"f (Hz)", "K"}]
```
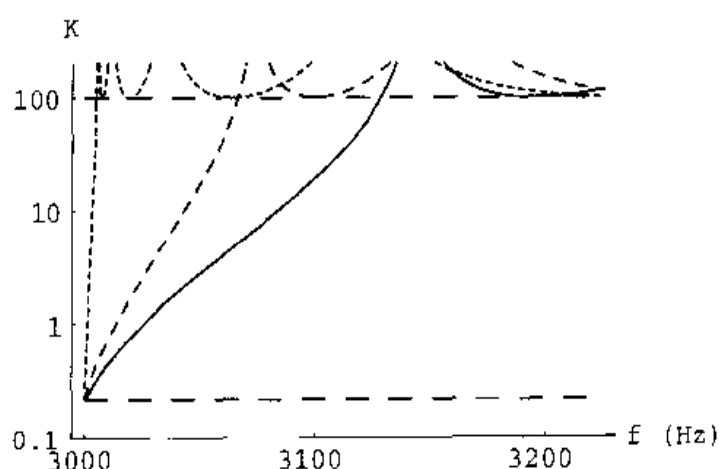
```
, PlotStyle -> {Dashing[{0.04}],
                Dashing[{0.04}],
                Dashing[{}],
                Dashing[{0.02}],
                Dashing[{0.01]}
                }
, Ticks -> {{3000, 3100, 3200}, {0.1, 1, 10, 100}}
, PlotRange -> {0.1, 200}];
```




■ A.7.12 Design D3b

```
Plot[Evaluate[{Kp
                , Ke[ 8, amin8,  emax, f/fpmax8]
                , Ke[ 9, amin9,  emax, f/fpmax9]
                , Ke[13, amin13, emax, f/fpmax13]
                }],
, {f, 0, Fp}
, AxesLabel -> {"f (Hz)", "K"}
, PlotStyle -> {Dashing[{0.04}],
                Dashing[{}],
                Dashing[{0.02}],
                Dashing[{0.01]}
                }
, Ticks -> {{1000, 2000, 3000}, {0, 0.1, 0.2}}
, PlotRange -> All];
```

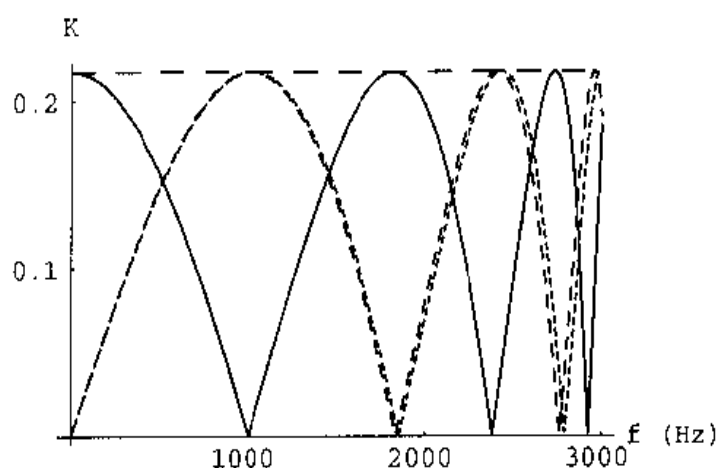

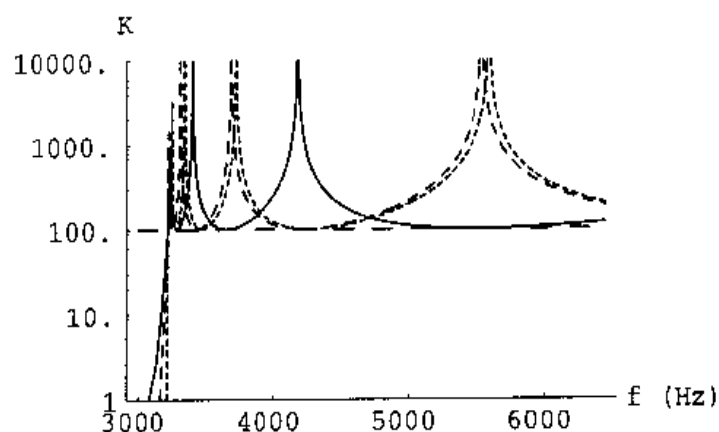
```
LogPlot[Evaluate[{{Ks
    , Ke[ 8, amin8,  emax, f/fpmax8]
    , Ke[ 9, amin9,  emax, f/fpmax9]
    , Ke[13, amin13, emax, f/fpmax13]
}}, {f, Fp, 2*Fs}
, AxesLabel -> {"f (Hz)", "K"}
, PlotStyle -> {Dashing[{0.04}],
    Dashing[{}],
    Dashing[{0.02}],
    Dashing[{0.01]}]
, Ticks -> {{3000, 4000, 5000, 6000}, Automatic}
, PlotRange -> {1, 10^4}];
```



```
LogPlot[Evaluate[{{Kp, Ks
    , Ke[ 8, amin8,  emax, f/fpmax8]
    , Ke[ 9, amin9,  emax, f/fpmax9]
    , Ke[13, amin13, emax, f/fpmax13]
}}, {f, Fp, Fs}
, AxesLabel -> {"f (Hz)", "K"}]
```



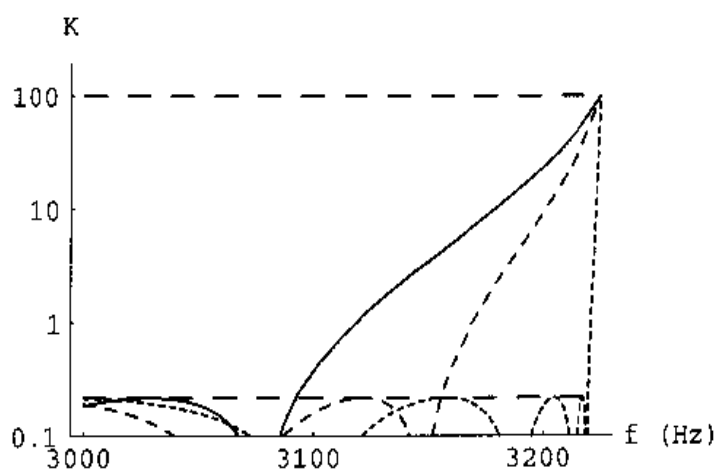
```
, PlotStyle -> {Dashing[{0.04}],
                Dashing[{0.04}],
                Dashing[{}],
                Dashing[{0.02}],
                Dashing[{0.01]}
                }
, Ticks -> {{3000, 3100, 3200}, {0.1, 1, 10, 100}}
, PlotRange -> {0.1, 200}];
```




■ A.7.13 Design D4a

```
Plot[Evaluate[{Kp
                , Ke[ 8, amax8,  emax, f/Fp]
                , Ke[ 9, amax9,  emax, f/Fp]
                , Ke[13, amax13, emax, f/Fp]
                }],
, {f, 0, Fp}
, AxesLabel -> {"f (Hz)", "K"}
, PlotStyle -> {Dashing[{0.04}],
                Dashing[{}],
                Dashing[{0.02}],
                Dashing[{0.01]}
                }
, Ticks -> {{1000, 2000, 3000}, {0, 0.1, 0.2}}
, PlotRange -> All];
```

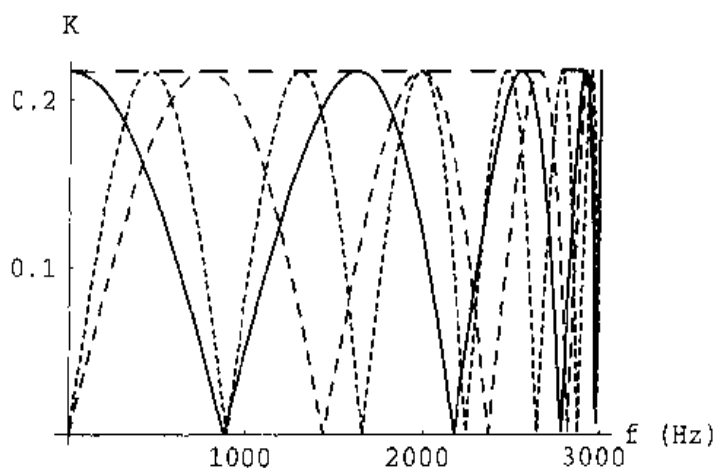

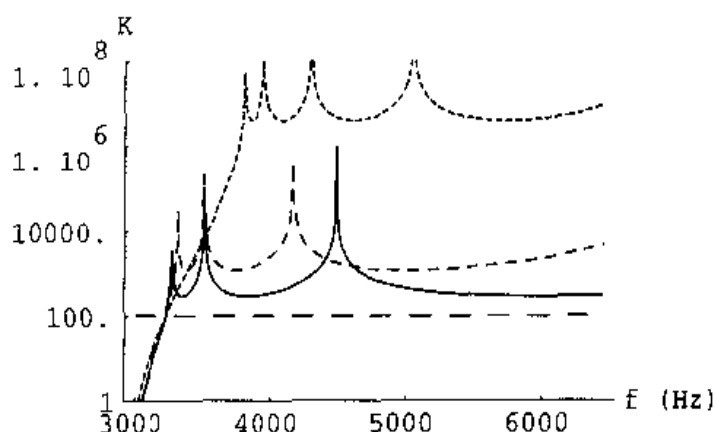
```
LogPlot[Evaluate[{Ks
    , Ke[ 8, amax8, emax, f/Fp]
    , Ke[ 9, amax9, emax, f/Fp]
    , Ke[13, amax13, emax, f/Fp]
}], {f, Fp, 2*Fs}
, AxesLabel -> {"f (Hz)", "K"}
, PlotStyle -> {Dashing[{0.04}],
    Dashing[{}],
    Dashing[{0.02}],
    Dashing[{0.01}]
}
, Ticks -> {{3000, 4000, 5000, 6000}, Automatic}
, PlotRange -> {1, 10^8}];
```



■ A.7.14 Design D4b

```
Plot[Evaluate[{Kp
    , Ke[ 8, amax8, emin8, f/(Fs/amax8)]
    , Ke[ 9, amax9, emin9, f/(Fs/amax9)]
    , Ke[13, amax13, emin13, f/(Fs/amax13)]
}], {f, 0, Fp}
```
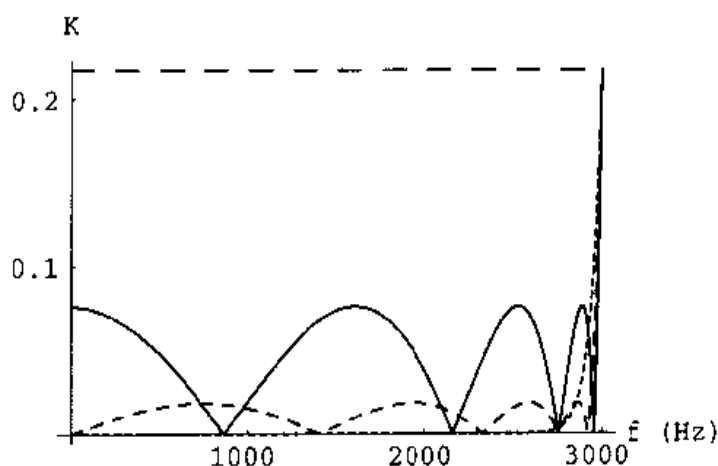
```
, AxesLabel -> {"f (Hz)", "K"}
, PlotStyle -> {Dashing[{0.04}],
                Dashing[{}],
                Dashing[{0.02}],
                Dashing[{0.01]}
                }
, Ticks -> {{1000, 2000, 3000}, {0, 0.1, 0.2}}
, PlotRange -> All];
```



```
LogPlot[Evaluate[{Ks
                , Ke[ 8, amax8, emin8, f/(Fs/amax8)]
                , Ke[ 9, amax9, emin9, f/(Fs/amax9)]
                , Ke[13, amax13, emin13, f/(Fs/amax13)]
                }],
, {f, Fp, 2*Fs}
, AxesLabel -> {"f (Hz)", "K"}
, PlotStyle -> {Dashing[{0.04}],
                Dashing[{}],
                Dashing[{0.02}],
                Dashing[{0.01]}
                }
, Ticks -> {{3000, 4000, 5000, 6000}, {1, 10, 100}}
, PlotRange -> {1, 10^3}];
```

